


Exam. Level	BE	Back	Full Marks	80
Programme	BEL,BEX,BEI,BCT	Pass Marks	32	
Year / Part	II / I	Time	3 hrs.	

**Subject:** - Electronic Devices and Circuits (EX 501)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



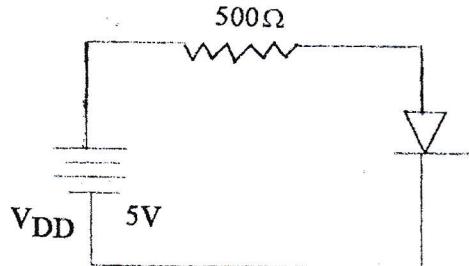1. What is Zener breakdown? Describe the Zener diode as a voltage regulator with circuit diagram and IV characteristic curve. [5]
2. In the given circuit the diode used has its  $\eta = 1.74$  and it conducts 1mA at forward bias voltage of 0.7 V. Find the current flow in the circuit. [5]



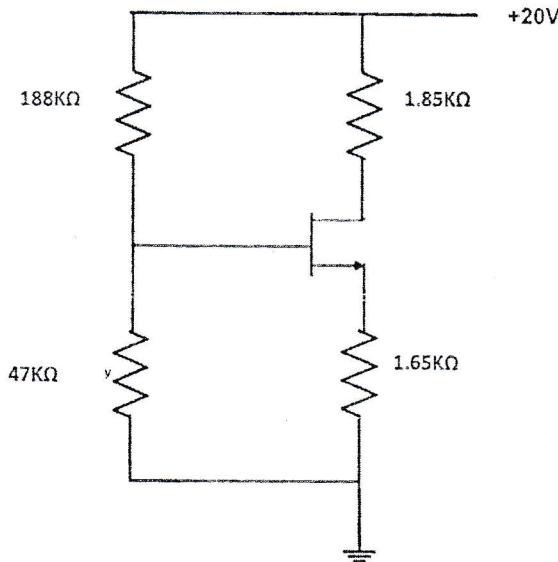3. Design CC amplifier using  $\beta$  independent voltage divider biasing circuit using appropriate guideline. Given:  $V_{CC} = 20V$ ,  $I_{CQ} = 2mA$  and  $\beta = 100$ . Use firm biasing. Derive its voltage gain. [8+2]
4. Draw Hybrid  $\pi$  and T model. Derive the relationship between  $r_\pi$  and  $r_e$ . [3+3]
5. Describe the construction and working principle of EMOSFET with the help of drain characteristics curve and mathematical expressions. [8]
6. Find the drain current( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for the following circuit. Given parameters are :  $V_t = 1$  V and  $k = 0.5\text{mA/V}^2$ . [8]



7. Draw the circuit diagram of transformer coupled class B push-pull amplifier. And show that the maximum efficiency is  $25\pi\%$ . [2+4]
8. What are the applications of tuned amplifiers? Determine its 3 dB Bandwidth, Resonance frequency and Quality factor. [2+6]
9. Explain the operation of RC Phase shift oscillator and derive the condition for the sustained oscillation. [3+4]
10. Draw the circuit diagram of Colpitts oscillator. Derive its frequency of oscillation. [2+4]
11. Describe the band gap voltage reference source with the help of a relevant circuit. Compare band gap voltage reference source with Zener diode. [4+2]
12. Design a voltage regulator to give output voltage from 7 V to 21 V using LM317. [5]

\*\*\*




TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
Examination Control Division  
2079 Baishakh

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI	Pass Marks	32
Year / Part	BCT II / I	Time	3 hrs.

**Subject:** - Electronics Devices and Circuits (EX 501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

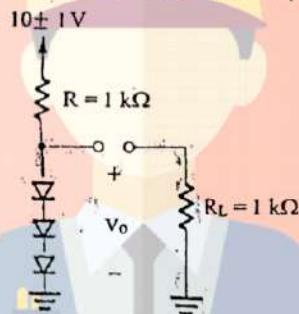1. A string of three diodes is used to provide a constant voltage of about 2.1 v. Calculate the change in this regulated voltage caused by (i) a  $\pm 10\%$  change in the power supply voltage; (ii) connection of a  $1\text{ k}\Omega$  load resistance. Assume  $\eta = 2$ . [3+2]




2. A zener diode exhibits a constant voltage of 5.6 V for currents greater than five times the knee current.  $I_{zk}$  is specified to be 1mA. The zener is to be used in the design of a shunt regulator fed from a 15V supply. The load current varies over the range of 0 mA to 15 mA. Find a suitable value for the resistor R. What is the maximum power dissipation of the zener diode? [3+2]
3. Design voltage divider CE amplifier (without emitter bypass capacitor). Given: Transistor BC 547B having  $\beta = 295$ ,  $I_c = 1.5 \text{ mA}$  and  $V_{cc} = +9\text{V}$ .
- Is this the best Q point? Why?
  - Calculate its input impedance and voltage gain.
  - What is the maximum peak voltage of the signal that can be applied to the input of this amplifier to ensure the transistor is always in active region? [5+2+3+2]
4. Draw Ebers-Moll (EM) model of BJT and write expression of collector current for active region. [5]

## ← 2079 Baisakh(Back) ↓

Q. Find Q point and show it graphically.

[6+2]

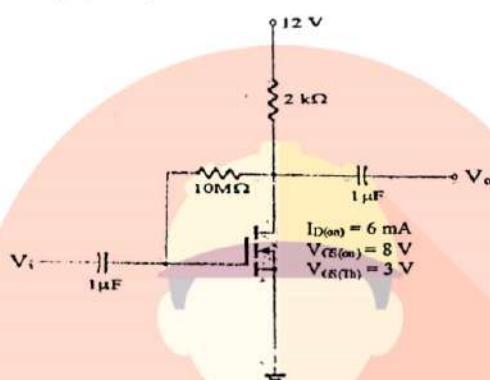

6. Explain the working of n channel DMOSFET with characteristics curves. Derive an expression for JFET transconductance.

[6+3]

7. It is required to design a class B power Amplifier to deliver an average power of 20 W to an  $8\ \Omega$  load. The power supply is to be selected such that  $V_{cc}$  is about 5 V greater than the peak output voltage. This avoids transistor saturation and associated nonlinear distortion, and allows for including short circuit protection circuitry. Determine the supply voltage required, the peak current drawn from each supply, the total supply power, and the power conversion efficiency. Also determine the maximum power that each transistor must be able to dissipate safely.

[1+1+2+2]

8. Derive general efficiency of series fed Class A power amplifier.

[6]

9. Explain the working principle of crystal oscillator with diagrams operating in both parallel and series resonance mode.

[4+2+2]

10. State Barkhausen Criteria for sinusoidal oscillation. Is it possible to obtain 50% duty cycle square wave from 555 timer Astable Multivibrator? How?

[2+3]

11. Explain the working of transistor series voltage regulator with current limiting element.

[6]

12. Design variable DC voltage regulator using LM 317 to get (5-9) volts output.

[5]

\*\*\*


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



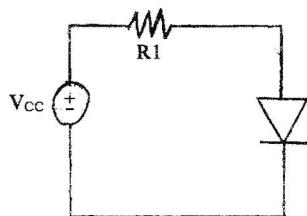1. What is Dc load line? Find operating point for the diode circuit graphically using load line method. [1+4]
2. In the circuit given below the DC power supply  $V_{CC} = 10$  V is superimposed with 60 Hz sinusoid of 1 V peak to peak amplitude. Calculate the amplitude of the sine wave signal appearing across the diode for the case  $R_1 = 10 \text{ k}\Omega$ . Assume the constant voltage drop of 0.7 V in the diode. [5]



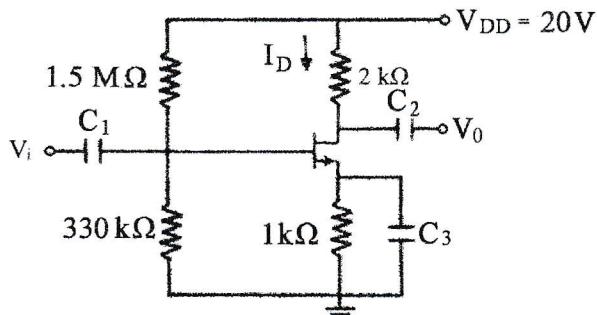3. Why voltage divider biasing called  $\beta$  independent? Design common emitter Amplifier using  $\beta$  independent dc biasing method with appropriate guideline. Given parameters:  $V_{CC} = 24$  VDC,  $I_C = 1.5$  mA,  $\beta = 150$ . [1+4+2+2]
4. What is the significance of bypass capacitor in CE amplifier? Draw the small signal model of voltage divider bias for emitter bypassed capacitor CE amplifier circuit and find its input impedance, output impedance and voltage gain. [2+6]
5. Explain construction and working principle of N channel Depletion type MOSFET with the help of drain characteristics and transfer characteristics. [8]
6. Find  $I_D$  and  $V_{DS}$  for the given circuit. Given data are  $V_P = -5.5$  V,  $I_{DSS} = 10$  mA and assume all the capacitors are ideal and check whether transistor is operating in pinch off region or not? [8]




7. Draw the circuit diagram of class B push-pull amplifier. Derive its general efficiency and maximum efficiency. [8]
8. Draw the circuit diagram of class A series fed amplifier and its corresponding characteristic graph. And, find its general efficiency. [3+4]
9. Draw the circuit diagram of op-amp Wein Bridge oscillator. Derive its frequency of oscillation. [2+4]
10. Draw the circuit diagram of Hartley oscillator. Derive its frequency of oscillation. [6]
11. Design DC voltage regulator using LM 317 to get 6-15V output. [6]
12. Draw standard series DC voltage regulator circuit and find its voltage stability factor ( $S_v$ ). [4]

TRIBHUVAN UNIVERSITY  
 INSTITUTE OF ENGINEERING  
**Examination Control Division**  
 2078 Bhadra


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)

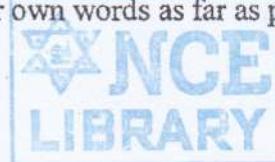
- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



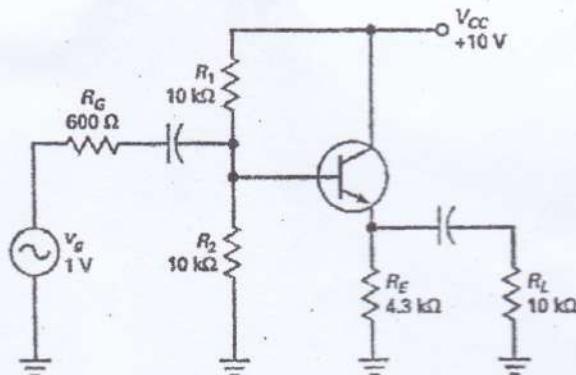1. Explain the reverse break down region in zener diode. "Zener diode acts as a voltage reference element" Justify the statement from IV characteristic curve. [5]
2. A diode conducts 1mA at 20°C. If it is operated at 100°C, what will be its current? Given data are  $\eta = 1.6$  and negative temperature coefficient value = -2.2 mV/°C. [5]
3. Show the importance of transistor bias stabilization. Design voltage divider bias (common collector configuration) to get  $I_{CQ} = 1.5$  mA. Assume power supply voltage  $V_{CC} = 15V$  and beta of transistor is 110. [3+5]
4. Why BJT is called bipolar and FET is called unipolar device? Derive mathematically the transconductance of MOSFET. [2+3]
5. The bipolar junction transistor parameters for the circuit in figure below are  $\beta = 200$  and  $V_A = \infty$ . Determine the input resistance, output resistance and overall voltage gain of the circuit. [8]



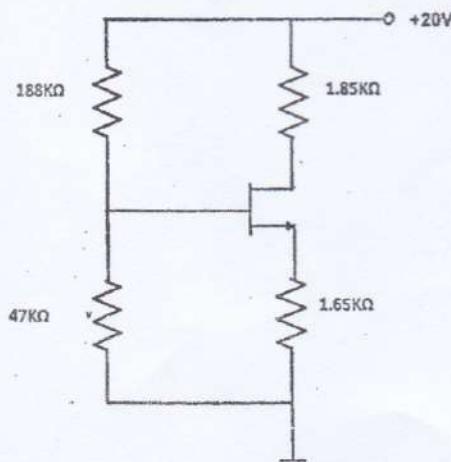6. Describe the physical structure of N-channel JFET and explain its working principal and characteristics clearly marking the various regions of operation. [2+6]
7. Find the drain current ( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for the following circuit. Given parameters are:  $V_t = 1$  V and  $k = 0.5$  mA/V<sup>2</sup>. [8]



8. Draw the circuit diagram of transformer coupled class B push-pull amplifier stage. And find its maximum efficiency. Define cross over distortion in class B amplifier. [2+4+2]
9. Draw the circuit diagram of Quasi complementary-symmetry class AB amplifier using diodes. [3]
10. When are tuned amplifiers used? Draw the circuit diagram of class-A tuned amplifier and its frequency response graph. [2+3]
11. Draw Wien Bridge oscillator circuit and derive the expression for frequency of oscillation and gain of amplifier circuit. [1+3+2]
12. Describe the operation of precision half wave rectifier with circuit diagram. [4]
13. Why transistor series regulator has lower efficiency? Explain the operation of voltage regulator using band gap voltage reference. [2+5]

\*\*\*


Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



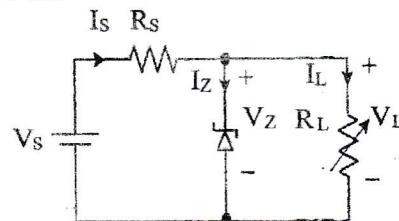1. Explain the small signal model of PN junction diode and derive the expression for its dynamic resistance. [5]
2. Determine the Range of load  $R_L$  that will maintain the zener diode load voltage  $V_L$  at 5V. Given  $V_S = 10$  V,  $R_S = 100 \Omega$ ,  $I_{ZM} = 30$  mA. [5]



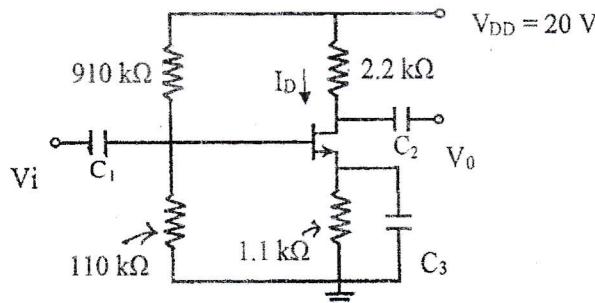3. Design a voltage divider type dc biased CE amplifier to obtain  $\beta$  independent biasing. Use appropriate guidelines to support your design. Given  $V_{CC} = 12$  V DC,  $I_C = 2$  mA and  $\beta = 150$ . [7]
4. Derive the expression for  $R_{in}$ ,  $R_{out}$ ,  $A_v$  and  $A_i$  in CE capacitor bypassed amplifier. [8]
5. Describe the construction and working principle of EMOSFET with the help of drain characteristics curve and mathematical expressions. [8]
6. Find  $I_D$  and  $V_{DS}$  for the given circuit. Given data are  $V_P = -3.5$  V,  $I_{DSS} = 10$  mA and assume all the capacitors are ideal and check whether transistor is operating in pinch off region or not? [7]




7. Draw the circuit diagram of transformer coupled class B push-pull amplifier and show that the maximum efficiency is  $25\pi\%$ . [7]
8. When are tuned amplifiers used? Draw class A tuned amplifier circuit and find its 3 dB bandwidth. [7]
9. Explain working of RC phase shift oscillators and derive the frequency of its oscillation. [6]
10. Draw standard series DC voltage regulator circuit and find its voltage stability factor ( $S_V$ ). [6]
11. Design a voltage regulator to give output voltage from 7V to 21V using LM317. [5]
12. Write short notes on:
  - Ebers Moll model
  - Transconductance of JFET
  - Crossover distortion

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**  
2076 Chaitra


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)

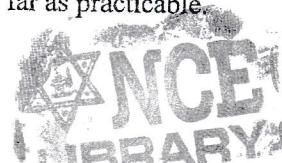
- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



- Define Q-point in pn junction diode operation. Show it graphically with necessary derivations. Differentiate between avalanche and zener break down. [3+2]
- The 6.8 V zener diode is specified to have  $V_Z = 6.8$  V at  $I_Z = 5$  mA,  $r_Z = 20\Omega$  and  $I_{ZK} = 0.2$  mA. The supply voltage  $V^+$  is nominally 10V but can vary by  $\pm 1$  V. Find  $V_0$  with no load and with  $V^+$  at its nominal value. Find the change in  $V_0$  resulting from connecting a load resistance  $R_L$  that draws a current  $I_L = 1$  mA. What is the minimum value of  $R_L$  for which the diode still operates in the breakdown region? [2+1+2]

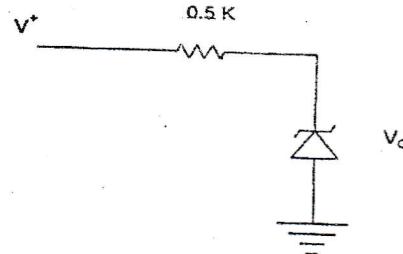

- Design  $\beta$  independent type dc biased common collector amplifier, and find its current gain and input resistance. Given parameters:  $V_{CC} = 20$  VDC,  $I_C = 2$  mA and  $\beta = 100$  and use firm biasing method. [8]
- Draw common emitter transistor amplifier circuit (emitter bias with unbypassed emitter capacitor) and find its output impedance and voltage gain. Write application of common base amplifier. [4+3+1]
- Describe the working principle of N-channel Depletion type MOSFET with the help of  $I_D$  vs  $V_{DS}$  characteristics and transfer characteristics curves. Find the condition and expression for it to operate in active mode of operation and write the expression for drain current. [5+2+1]
- Write about JFET as a voltage controlled resistor with practical application. [4]
- Find  $I_{DQ}$  and  $V_{GSQ}$  from the following circuit. [5]

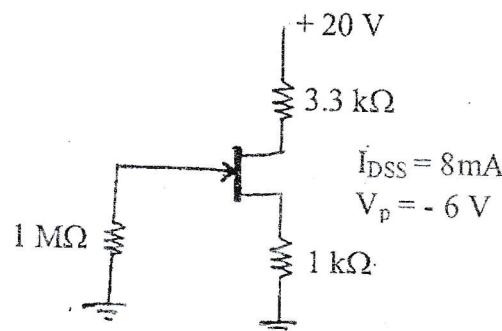

- 
8. Draw the circuit diagram of class A series fed amplifier and its corresponding characteristic graph. And, find its general efficiency. [3+3]
  9. Draw the circuit diagram of Complementary-Symmetry class-AB amplifier using Darlington pair transistors. [3]
  10. Describe about tuned amplifier and derive the expression for the 3dB bandwidth of the amplifier. [5]
  11. Differentiate between synchronous and stagger turned amplifier. [3]
  12. Draw voltage controlled oscillator circuit using IC 555 and derive expression for frequency of oscillation. [6]
  13. Among Hartley and Colpitts LC oscillator, which one do you choose to implement in FM stations to generate carrier wave signal? Why? Draw its circuit diagram. [5]
  14. Draw the standard series DC voltage regulator circuit and find its voltage stability factor( $S_v$ ). [5]
  15. Design a 5V to 20V variable dc voltage regulator using IC LM317. [4]

\*\*\*

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
Examination Control Division  
2076 Ashwin


Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT.	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



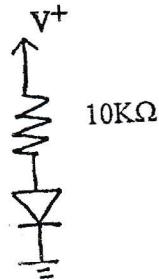
1. Differentiate between avalanche and zener breakdown. Draw V-I characteristic curve of zener diode and briefly explain about it. [3+2]
2. In the given circuit, the power supply  $V^+$  has a dc value of 10V on which is superimposed a 50 Hz sinusoid of 1V peak amplitude. Calculate both the dc voltage of the diode and amplitude of the sine-wave signal appearing across it. Assume the diode to have a 0.7V at 1 mA current and  $\eta=2$ . [5]



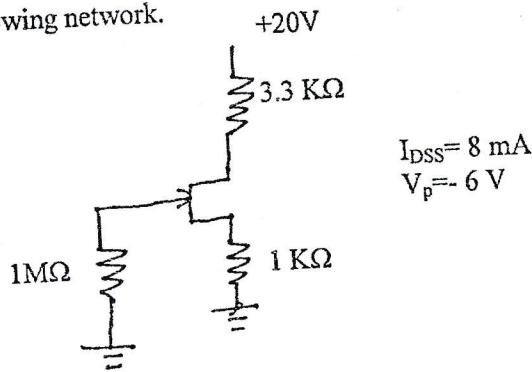3. Design  $\beta$  independent type of dc biased common collector amplifier, and find its voltage gain and input resistance. Given parameters:  $V_{cc} = 20$  VDC,  $I_c = 2\text{mA}$  and  $\beta = 100$  and use firm biasing method. [8]
4. Describe in brief the operation of BJT as a switch in cut off and saturation region. [4]
5. Explain about working principle of N-channel DMOSFET with its construction, characteristics curves and characteristic equation. [7]
6. For the faithful amplification of signal, selection of operating point is utmost importance. Justify the above statement. Derive transconductance of bipolar junction transistor. [3+4] [7]
7. Determine Q point for the following network. [7]



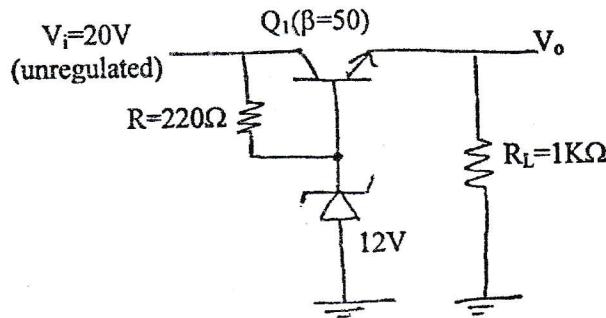8. Draw the circuit diagram of the Hartley Oscillator and derive its frequency of oscillation. [6]
9. Draw the circuit diagram of class A series fed amplifier and its corresponding characteristics graph. And find its general efficiency. [3+3]
10. Explain about the operation of voltage controlled oscillator (VCO) using 555 timer IC and derive its frequency of oscillation. [8]
11. Draw the circuit diagram of Complementary-Symmetry Class-AB amplifier using Darlington pair transistors. [3]
12. Calculate the output voltage and the zener current in the regular circuit as shown in figure below for  $R_L=1\text{ K}\Omega$  and  $R=220\Omega$ .  $V_z=12\text{V}$ . [5]



13. Draw series voltage regulator with current limiting circuit and explain how this protection circuit works? [6]
14. Briefly explain about Precision half wave rectifier with circuit diagram. [3]

\*\*\*

TRIBHUVAN UNIVERSITY  
 INSTITUTE OF ENGINEERING  
**Examination Control Division**  
 2075 Chaitra


Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX 501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



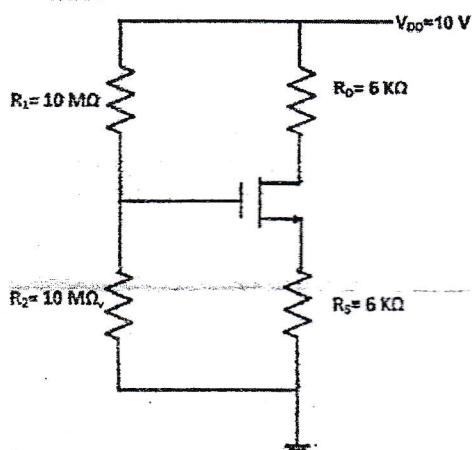1. Find the operating point of the diode circuit graphically using load line method. [5]
2. Design DC voltage regulator for 6V output. Given data are  $V_2=6V$  at  $I_z=20mA$ ,  $I_{zx}=2mA$ ,  $P_{zmax}=500mW$  and  $r_z=10\Omega$ . The nominal input voltage is  $15V+30\%$  DC. Find the maximum current it can deliver to the load. [5]
3. Design a common base amplifier circuit using  $\beta$  independent method. Given parameters are  $V_{cc}=15V$ ,  $I_E=1.5mA$ ,  $\beta=100$  and input and output impedances are comparatively large. Use appropriate guideline to support your design. [7]
4. Why common collector amplifier is known as emitter follower? Draw its ac equivalent circuit to find its input resistance and voltage gain. [1+6]
5. Draw and describe the Ebers Moll model for BJT. [4]
6. Draw the cirucuit diagram of the Colpitts Oscillator and derive its frequency of Oscillation. [6]
7. Find the drain current ( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for the following circuit. Given parameters are:  $V_t=1 V$  and  $k=0.5 \text{ mA/V}^2$ . [7]



8. Describe the construction and working principal of N-channel JFET with the help of characteristics curve and mathematical expression. [7]

9. Define crossover distortion in class B amplifier. Draw quasi-complementary symmetry class AB amplifier. And explain how crossover distortion is eliminated in class AB amplifier. [7]
10. Draw the circuit diagram of Class A tuned amplifier and determine the range of frequency in which it gives maximum gain within 3 dB range? [6]
11. Design a DC voltage regulator for 3V to 12V output using LM317. [5]
12. Define the term multivibrator. Explain the operation of op-amp based astable multivibrator for square wave with the help of circuit diagram and waveforms and also determine its frequency of oscillation. [8]
13. Draw the standard series DC voltage regulator circuit and find its voltage stability factor( $S_v$ ). [6]

\*\*\*




Exam.	Back
Level	BE
Programme	BEX, BCT, BEL
Year / Part	II / I
Full Marks	80
Pass Marks	32
Time	3 hrs.


**Subject:** - Electronic Devices and Circuits (EX501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

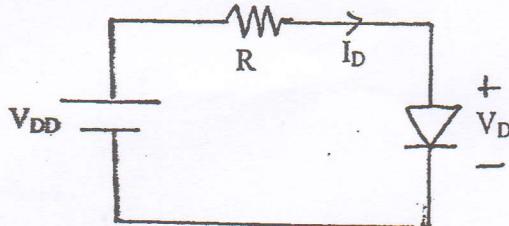1. Derive the expression for dynamic resistance of pn junction diode. [5]
2. Determine the current  $I_D$  and the diode voltage  $V_D$  with  $V_{DD}=5$  V and  $R=1K\Omega$ . Assume that the diode has a current of 1 mA at a voltage of 0.7 V and that its voltage drop changes by 0.1 V for every decade change in current. [5]



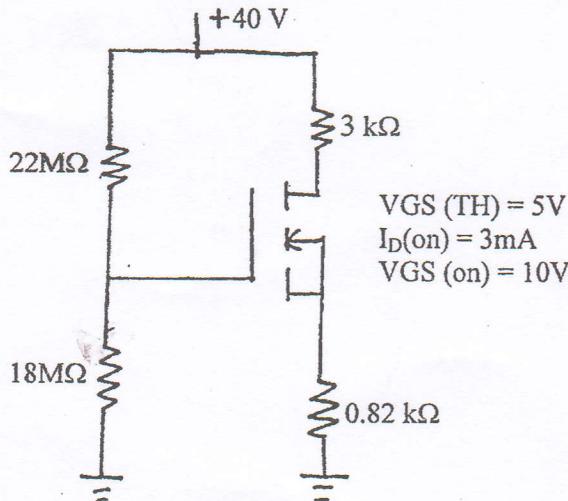3. Design voltage divider biased common emitter BJT amplifier to get voltage gain of -90. Assume  $\beta = 100$  and  $V_{cc}=+12V$ . [8]
4. Derive input impedance, output impedance and voltage gain of common collector BJT amplifier. [8]
5. Explain the construction and operation of E-MOSFET with characteristics curve and mathematical expression. [7]
6. Derive mathematical definition of JEFET transconductance. [4]
7. Find  $I_{DQ}$  and  $V_{DSQ}$  from the following circuit. Show Q point graphically. [5+3]



8. Derive general efficiency of class B amplifier. [5]
9. Draw the circuit diagram of Darlington complementary-symmetry class AB amplifier using diodes. [3]
10. Derive maximum efficiency of transformer coupled class A amplifier. [5]
11. Draw astable multivibrator circuit using IC 555 and derive expression for frequency of oscillation. [6]
12. Explain working principle of RC phase shift oscillator with necessary expressions and circuit diagram. [6]
13. Explain the operation of voltage regulator using band gap voltage reference. [6]
14. Design a (5-15)V variable dc voltage regulator using LM 317 IC. [4]


\*\*\*

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.


**Subject:** - Electronic Devices and Circuits (EX501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

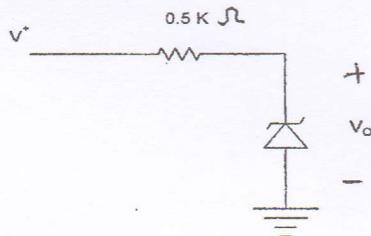1. The leakage current of a silicon diode is  $I_S = 10^{-9}$  A at  $25^\circ\text{C}$ , and the emission coefficient is  $\eta = 1.6$ . The operating junction temperature is  $T_j = 60^\circ\text{C}$ . Determine (i) the leakage current  $I_S$  and (ii) the diode current  $I_D$  at  $V_D = 0.8$  V. [4]
2. The 6.8V zener diode is specified to have  $V_z = 6.8$  V at  $I_z = 5$  mA,  $r_z = 20 \Omega$  and  $I_{zK} = 0.2$  mA. The supply Voltage  $V^+$  is nominally 10 V but can vary by  $\pm 1$  V. Find  $V_0$  with no load and with  $V^+$  at its nominal value. Find the change in  $V_0$  resulting from connecting a load resistance  $R_L$  that draws a current  $I_L = 1$  mA. What is the minimum value of  $R_L$  for which the diode still operates in the breakdown region? [2+2+2]




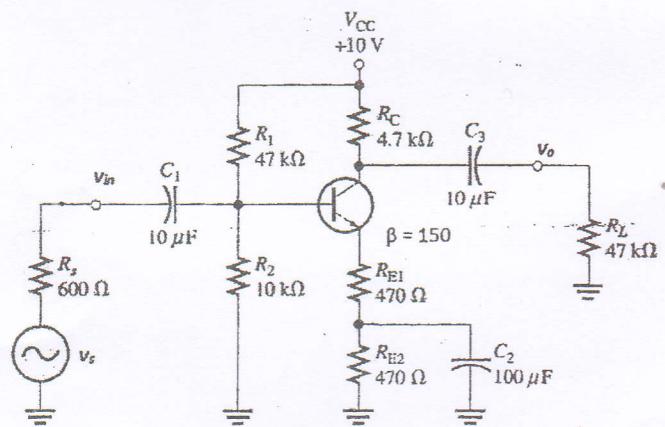3. Determine the input resistance, output resistance and overall voltage gain of the circuit given below: [8]



4. Find terminal currents of BJT using Ebers-Moll Model. Write applications of different BJT configurations. [5+3]
5. Explain the construction and operation of D-MOSFET with characteristics curve and mathematical expression. [8]

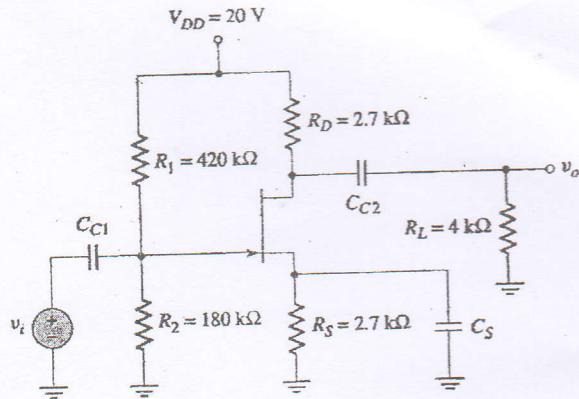6. Find the DC operating point of JFET circuit given below. Given parameters  $I_{DSS} = 12 \text{ mA}$  and  $V_P = -4V$ . [8]



7. Derive maximum efficiency of series fed class A amplifier. [6]
8. Derive bandwidth of tuned amplifier. Write its applications. [6]
9. For a class B amplifier providing a 14V peak signal to  $16 \Omega$  load and a power supply of  $V_{cc} = 24V$ , determine input power, output power and circuit efficiency. [4]
10. Draw voltage controlled oscillator circuit using IC 555 and derive expression for frequency of oscillation. [6]
11. Draw the circuit diagram of half wave precision rectifier and explain the operation. [4]
12. Define voltage regulator. Explain the series voltage regulator with current limiting element. [1+5]
13. Explain working principle of WIEN BRIDGE oscillator with necessary expressions and circuit diagram. [6]


\*\*\*

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.


**Subject:** - Electronic Device and Circuits (EX501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Scientific Calculator is allowed.
- ✓ Assume suitable data if necessary.

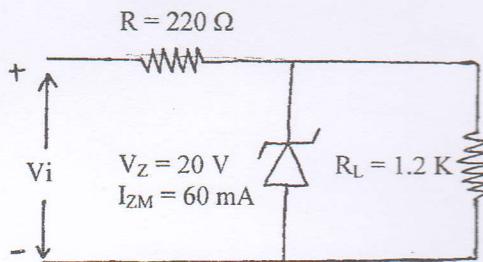1. Explain the small signal model of PN junction diode and drive its dynamic resistance. [2+4]
2. Determine the range of values of  $V_i$  that will maintain the Zener diode of figure below in ON state. [5]



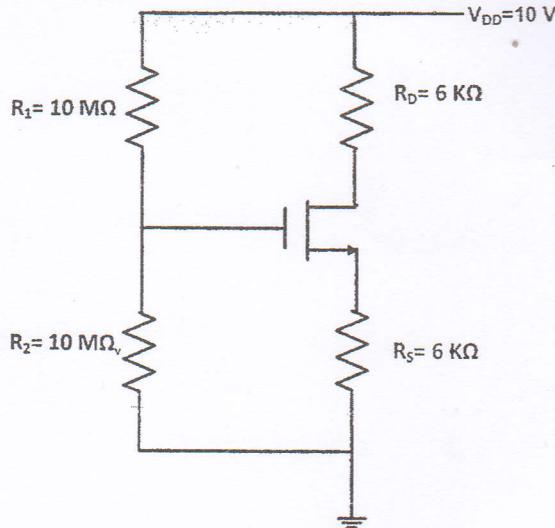3. Design  $\beta$  independent type DC biased common emitter amplifier with emitter resistance bypassed and find its voltage gain and input resistance. Given parameters  $V_{cc} = 24$ ,  $I_C = 2 \text{ mA}$ ,  $\beta = 90$ . Use appropriate guideline to have high input resistance. [8]
4. Describe in brief the operation of BJT as a switch in cut off and saturation region. [6]
5. Define transconductance ( $g_m$ ). Derive  $g_m$  for BJT. [1+3]
6. Explain the construction and operation of N channel enhancement type MOSFET with the help of drain characteristics and transfer characteristics. [8]
7. Find the drain current ( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for the following circuit. Given parameters are:  $V_t = 1 \text{ V}$  and  $k = 0.5 \text{ mA/V}^2$ . [6]



8. State the difference between BJT and FET. [2]
9. What is crossover distortion? Explain how it can be eliminated with necessary diagram. [2+4]
10. Draw the circuit diagram of tuned amplifier and derive the expression for the 3dB bandwidth of the amplifier. [6]
11. Define Barkhausen criteria for sinusoidal oscillation. Draw the circuit diagram of wien bridge oscillator and determine its frequency of oscillation. [2+6]
12. Describe Colpitt's oscillator with necessary circuit diagram. [5]
13. Draw the standard series DC voltage regulator circuit and find its voltage stability factor ( $S_v$ ). [6]
14. Design a 3.7 to 9V variable dc voltage regulator using IC LM317. [4]

\*\*\*

**Examination Control Division**


2073 Shrawan

Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.


**Subject:** - Electronic Devices and Circuits (EX501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

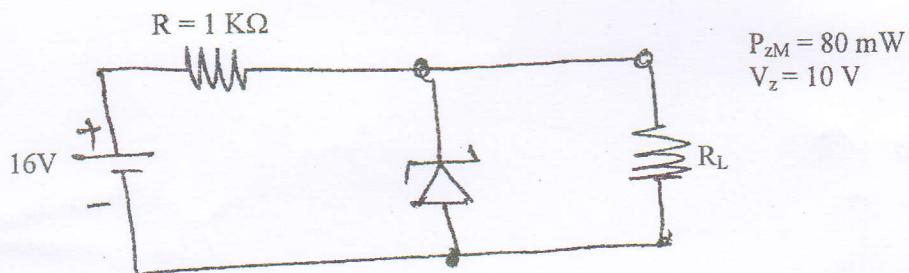1. Find operating point for the diode circuit graphically using load line method. [4]
2. Find the zener current from the given circuit if (i)  $R_L = 1.2 \text{ K}\Omega$  (ii)  $R_L = 3 \text{ K}\Omega$  [4]



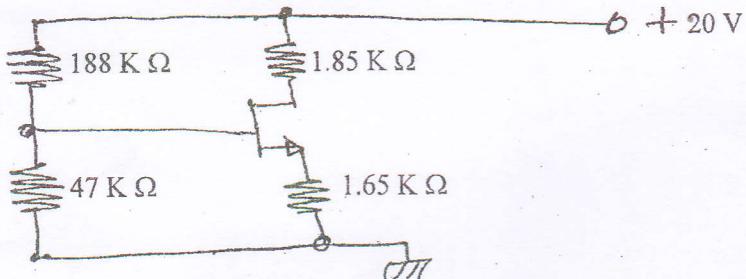3. Determine the input resistance and output resistance of CC BJT amplifier circuit. Why common collector configuration is used in amplifier circuit design. [2+2+2]
4. Describe the operation of BJT as switch with the help of Non-gate circuit. [4]
5. Derive expressions to obtain transconductance for BJT, JFET and MOSFET. Also prove that  $\gamma_\pi = (\beta + 1)\gamma_e$  [8]
6. The n-channel JFET in the figure below has  $I_{DSS} = 18 \text{ mA}$  and  $V_p = -5 \text{ V}$ . Determine the values of  $I_D$  and  $V_{DS}$ . [8]



7. Describe the working principle of N-channel EMOSFET with the help of its drain characteristics curve and necessary mathematical expressions. [6]

8. Determine the general efficiency of transformer coupled class B push pull amplifier.  
Draw the circuit diagram and its graph. [4+4]
9. Explain how class AB amplifier eliminates the cross over distortion. [3]
10. Draw the circuit diagram of LRC tuned class A amplifier and its frequency response  
graph and show that Bandwidth =  $\frac{1}{RC}$ . [3+3]
11. Explain the operation of AMV using 555 timer IC and derive its frequency of oscillation. [6]
12. Draw the circuit diagram of Hartley oscillator. [3]
13. Draw standard dcV regulator circuit and find its voltage stability factor. [4+4]
14. Design a DCV regulator for 3.7 V to 12 V output using LM317. [4]

\*\*\*


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	H / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits (EX501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. In the given circuit, the diode used has its  $n = 1.74$  and it conducts 1mA at forward bias voltage of 0.7 V. Find the current flow in the circuit. [4]

$$R = 500 \Omega$$

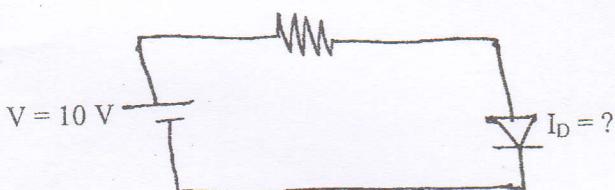


2. Design DC voltage regulator for 6V output. Given data are  $V_z = 6$  V at  $I_z = 20$  mA,  $I_{2k} = 2$  mA,  $P_{Zmax} = 500$  mw and  $r_z = 10\Omega$ . The nominal input voltage is  $15V \pm 30\%$  DC. Find maximum current it can deliver to the load. [4]

3. Design  $\beta$  independent type dc biased common collector amplifier and find its current gain and input resistance. Given parameters are:  $V_{CC} = 20$  V,  $I_C = 2$  mA and  $\beta = 100$ . Use firm biasing method. [8]

4. Draw the small signal model circuit for capacitor unbypassed CE amplifier and find its voltage gain and current gain. [8]

5. Describe the construction and working principle of N-channel JFET with the help of its drain characteristics curve and necessary mathematical expressions. [6]

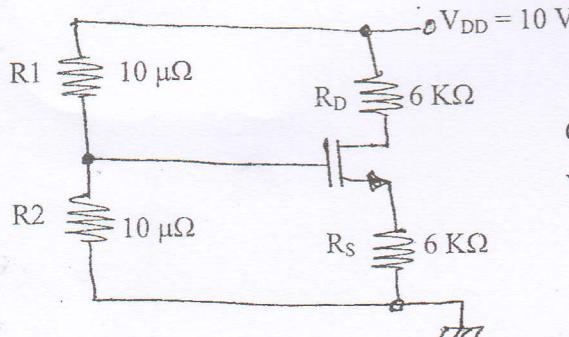6. For the circuit given below, find  $I_D$  and  $V_{DS}$ . Also determine its region of operation and small signal ac equivalent circuit. [3+3+2+2]



Given data are:  
 $V_t = 1$  V,  $k = 0.5 \frac{\text{mA}}{\text{V}^2}$

7. Draw the circuit diagram of transformer coupled class B push pull amplifier and its corresponding characteristic graph. And from graph prove that maximum efficiency is equal to 78.5%. Also find the condition when it has maximum loss. [3+3+3+3]
8. Draw the circuit diagram and its frequency response graph of LRC tuned class A amplifier. State its resonance frequency and band width (3dB). [1+1+1+1]
9. State Barkhausen criteria for sinusoidal oscillator. Is this principle applicable to RC oscillator using op-Amp? Why? If yes, determine the frequency of oscillations and the gain of the amplifier of the circuit. [2+1+4]
10. Explain the operation of AMV using 555 IC and derive its frequency of oscillation. [6]
11. Describe the bandgap voltage reference source with the help of a relevant circuit. Compare bandgap voltage reference source with zener diode. [4+2]
12. Draw the series dc voltage regulator with current limiting element and explain how it works. 7 [5]


\*\*\*

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.


**Subject: - Electronic Device and Circuits (EX501)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

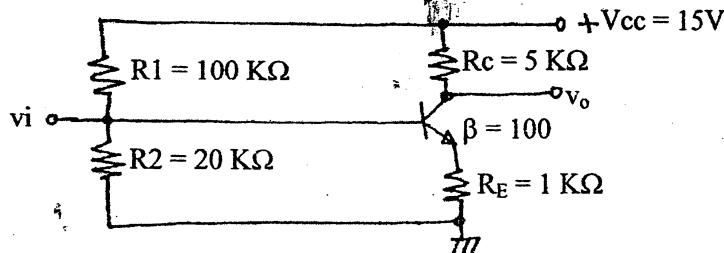1. Draw full wave bridge rectifier circuit with 5 ohm load resistor connected at its output. If input ac voltage is 10V, calculate the power dissipation in the load resistor (Assume diodes operate at forward voltage of 0.7V). [4]
2. Explain the small signal model of PN junction diode and derive the expression for AC or dynamic resistance. [2+4]
3. Draw the ac equivalent circuit for given circuit and find its input and output resistances. Assume  $\beta = 100$  for the BJT. [8]



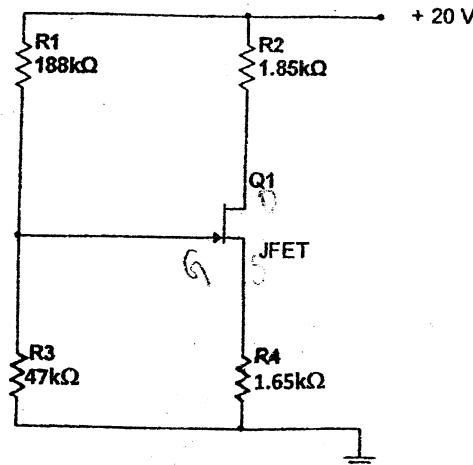4. Define transconductance ( $gm$ ). Derive  $gm$  for BJT [2+4]
5. Describe in brief the operation of BJT as a switch. [4]
6. Describe with necessary graphs and expressions the principle of operation of N-channel JFET. [6]
7. The n-channel JFET in the figure below has  $I_{DSS} = 18 \text{ mA}$  and  $V_p = -5\text{V}$ . Determine the values of  $I_D$  and  $V_{DS}$ . [8]



8. State the difference between BJT and FET [4]
9. Determine the general efficiency of Transformer Coupled Class-A power Amplifier. [6]
10. Draw the circuit diagram of Complementary-Symmetry Class-AB Amplifier. [2]
11. Calculate the efficiency of transformer coupled push pull Power Amplifier for a supply voltage of 20V and output of (i)  $V_P = 20V$  (ii)  $V_P = 16V$ . [3+3]
12. Draw Wien Bridge Oscillator circuit and derive the expression for frequency of Oscillation and gain of the amplifier circuit. [2+3+3]
13. Draw standard series dc voltage regulator and find its voltage stability factor ( $S_v$ ). [6]
14. Design a 4.2 V to 12 V variable dc voltage regulator using IC LM317. [4]
15. Draw the circuit diagram of square wave generator. [2]


\*\*\*

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.


**Subject:** - Electronic Devices and Circuit (Ex 501)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

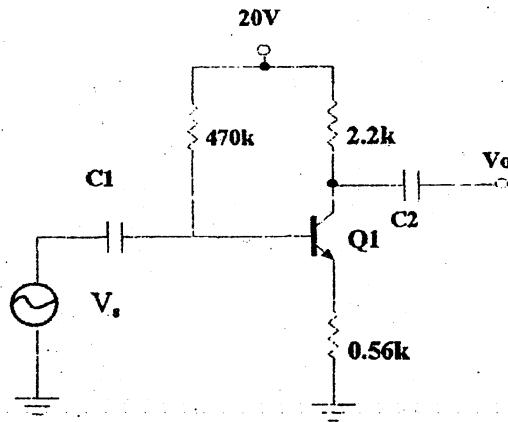1. Explain the large signal models of PN junction diode. [4]
2. A diode conducts 1mA at 20°C. If it is operated at 100°C, what will be its current? Given data are:  $\eta=1.8$  and negative temperature coefficient value =  $-1.8\text{mV}/^\circ\text{C}$ . [4]
3. For the figure shown below with  $\beta = 120$  find the a) input impedance (b) Output impedance (c) voltage gain (d) current gain. Use small signal model. [2+2+2+2]



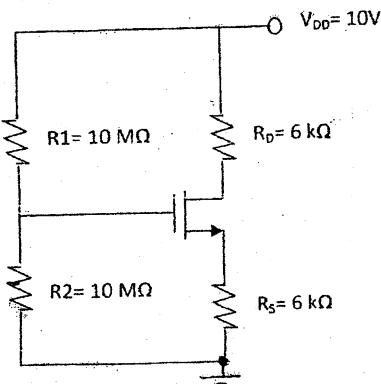4. Draw ac equivalent circuit of common collector amplifier. Find its input and output resistances. [2+3+3]
5. Describe the physical structural of N-channel JFET and explain its working principle and characteristics clearly marking the various regions of operation. [2+6]
6. Derive the expression to obtain the transconductance of E-MOSFET. [4]
7. Find the drain current ( $I_D$ ) and drain to source voltage ( $V_{DS}$ ) for the following circuit. Given parameters are:  $V_t = 1\text{V}$  and  $k = 0.5\text{mA/V}^2$ . [4]



8. Draw the circuit diagram of class B push pull amplifier with output transformer and explain how push pull action is achieved. Determine the general efficiency of class B push pull amplifier. [1+3+4]
9. Draw class A tuned amplifier circuit and derive the expression for 3dB bandwidth of the amplifier. [2+6]
10. Describe the operation of IC 555 as square wave oscillator and find its frequency of oscillation. [6+2]
11. Estimate voltage stability factor ( $S_v$ ) for standard series dc voltage regulator using BJT. Also, explain the operation of overload protection circuit that could be used in series voltage regulator circuit. [5+3]
12. A class B audio amplifier is providing 20V peak sine wave signal to  $8\Omega$  speaker with power supply of 25V ( $=V_{cc}$ ). At what efficiency is it operating? [4]
13. Define and explain the reverse breakdown effect in diodes. [4]


\*\*\*

Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / I	Time	3 hrs.

**Subject:** - Electronic Devices and Circuits

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

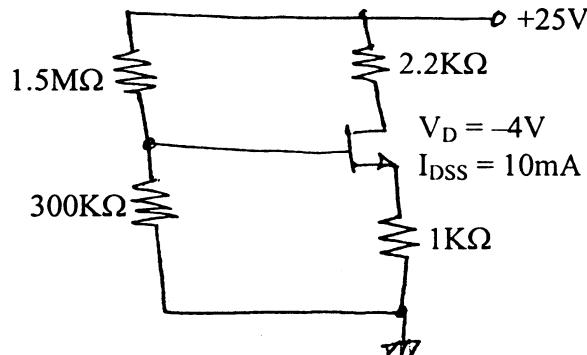1. Draw graphs of IV characteristics of ordinary PN junction diode and zener diode. Draw ac equivalent model for PN junction diode and derive its ac resistance. [7]
2. Define and explain reverse break down effect. [3]
3. Design  $\beta$ -independent type dc biased common collector amplifier, and find its current gain and input resistance. Given parameters are:  $V_{CC} = 20V$ ,  $I_C = 2mA$ ,  $\beta = 100$  and use firm biasing method. [8]
4. Derive an expression to find output resistance for emitter unbypassed common emitter amplifier circuit. [5]
5. Draw Ebers Moll model and ac equivalent T- model for BJT. [4]
6. Describe the principle of operation of EMOSFET with the help of IV characteristic curves and algebraic expressions. Also show its ac equivalent circuit model. [7]
7. Find  $I_D$  and  $V_{DS}$  for the given circuit. [5]



8. Derive an expression to find the transconductance for JFET. [2]
9. Draw standard series dc voltage regulator circuit and find its voltage stability factor ( $S_v$ ). [6]
10. Draw a voltage regulator circuit using IC LM317. [3]
11. Draw a circuit diagram for Bandgap reference voltage source. [3]
12. Define cross over distortion in class B amplifier. Draw quasi-complementary symmetry class AB amplifier. And explain how crossover distortion is eliminated in class AB amplifier. [7]
13. What is the maximum efficiency of class B amplifier? State the condition when it occurs. [4]
14. Why heat sink is necessary in power transistor? Explain with the help of thermal Ohm's law or thermal resistance method. [4]
15. State Barkhausen criteria and explain the principle of oscillation. [4]
16. Draw Wien Bridge Oscillator circuit and write the expression for frequency of Oscillation. [6]
17. Draw crystal oscillator circuit. [2]

21 TRIBHUVAN UNIVERSITY  
 INSTITUTE OF ENGINEERING  
**Examination Control Division**  
 2067 Mangsir

Exam.		Regular / Back	
Level	BE	Full Marks	80
Programme	BEL, BCT, BCT	Pass Marks	32
Year / Part	II / II	Time	3 hrs.

**Subject:** - Electronic Circuits I

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

- ✓ With the aid of  $i_D - v_{GS}$  curve, verify that the transconductance  $g_m$  of a MOSFET depends upon the dc bias point. [5]
- ✓ State why the resistors and capacitors are minimized in IC fabrication. [5]
- ✓ Explain how the voltage gain of difference amplifier would be larger when a current mirror is used at the load as compared to using only a simple resistance at the load. [6]
4. Draw emitter follower with voltage divider and current mirror dc level shifting circuits and which circuit performs better results and why? [2+2+3]
- ✓ Find the close loop input impedance of non inverting Op-amp. Derive the expression to reduce the effect of input offset current in an Op-amp. [4+3]
- ✓ For a non-inverting op-amp  $R_i = 1K\Omega$ ,  $R_f = 20 K\Omega$ ,  $V_{CC} = \pm 15$  volt. The op-amp has a slew rate of  $0.5V/\mu sec$ , and a saturation dropout voltage of 10%. Find maximum input voltage in RMS value at 10 KHz sine wave. [6]
- ✓ Draw circuit diagram of variable series voltage regulator with transistor error amplifier circuit and derive its voltage regulation factor,  $S_v$ . [2+5]
8. Design a regulator circuit diagram to obtain 16 VDC with input voltage of 25 VDC. [5]
9. Draw a circuit diagram of transformer coupled class B push pull amplifier clearly. And determine its maximum efficiency. [3+5]
- ✓ Discuss crossover distortion in push pull amplifier, and state how you can eliminate it. [6]
11. Define Barhausen Criteria for sinusoidal oscillation. Draw a circuit diagram of RC oscillator and derive its frequency of oscillation. [3+1+8]
- ✓ Draw the circuit diagram of triangular wave generator. Explain the operation of square wave generator circuit. [2+4]

\*\*\*

Exam.		Back	
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT	Pass Marks	32
Year / Part	II / II	Time	3 hrs.

**Subject:** - Electronic Circuits I

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. List out the advantages of monolithic IC as compared with discrete components. 4
2. Draw hybrid- $\pi$  model of BJT as a) voltage controlled current source, b) current controlled current source. 3+3=6
3. Draw a simple current mirror and describe its operation. What are the reasons for the output current of a simple current mirror not being exactly equal to the reference current? 2+4+4=10
4. Discuss the importance of active load and level shifting circuit in op-amps. 5+5=10
5. Define slew rate of an op-amp. A 10mV-10 kHz sine wave is input to an op-amp with a gain of 1000. Calculate the minimum slew rate that is required for the op-amp to produce an output without any distortion. (The sine wave and slew rate are related with the expression  $SR=2\pi fA$ ) 3+4=7
6. For an inverting op amp,  $R_i = 1k$ ,  $R_f = 10k$ ,  $V_{cc} = \pm 15$  V. The op amp has a slew rate of  $0.5$  V /  $\mu$ s, a saturation dropout voltage of 10% and gain bandwidth product of 1 MHz. Plot the gain and phase response of the circuit, and also show the output waveform when a 5 V peak to peak sine wave of 1 kHz frequency is used as the input to this circuit. 2+2+2=6
7. Define loading effect in unregulated power supply. Draw a series transistor zener diode voltage regulator, and state how this problem is taken care of by this circuit. 2+6=8
8. Compare zener diode with bandgap voltage reference. 4
9. How does cross over distortion occur in class B push pull amplifier? Discuss the change in effects of cross over distortion when the magnitude of the input signal is reduced, and when the frequency is decreased. What will you do to eliminate cross-over distortion? Discuss the impact of this remedy in terms of power dissipation. 3+2+2+3+2=12
10. Describe "Barkhausen Criteria" for oscillation. Write down the general expression for the gain of a feedback amplifier, and state the condition for oscillation. 5
11. Draw and explain the operation of CMOS inverter relaxation oscillator. 8

\*\*\*