

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2077 Chaitra

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BCE, BEL, BEX, BCT, BME, BAM, BIE, BAG, BGE, BAS	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


**Subject:** - Basic Electronics Engineering (EX 451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

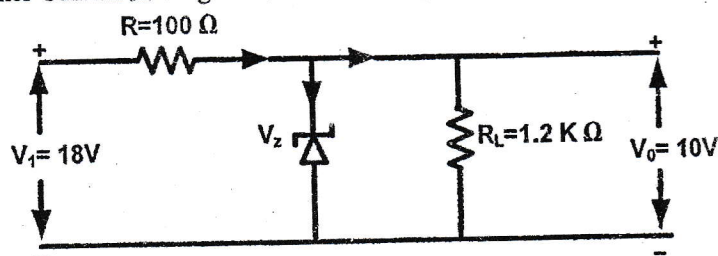
- Write the color coding of the following values of resistors: [4]  
 a)  $47 \pm 5\% \text{ k}\Omega$       b)  $548 \pm 10\% \Omega$
- Explain RC low pass filter with necessary derivations and diagrams. [4]
- Find the Zener Current in the given circuit when  $R_L = 1.2 \text{ k}\Omega$ . Assume  $V_Z = 10\text{V}$ . [4]



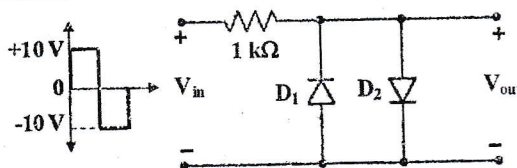- Find the output voltage waveform when the input is applied to the circuit as shown in the figure using silicon diodes. [4]



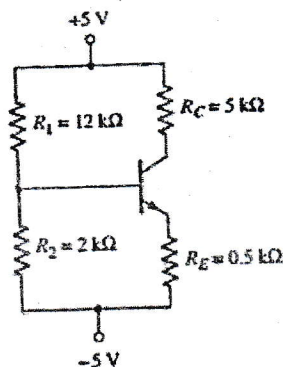- Describe the input and output characteristics of common emitter BJT configuration with the help of circuit diagram and graph with various region of operation. [6]
- Describe the construction and working principle of Depletion MOSFET with necessary diagrams. [5]
- Find collector current ( $I_C$ ) and collector emitter voltage ( $V_{CE}$ ) of the BJT circuit given below with  $\beta = 100$ . [5]



8. List out ideal characteristics of op-amp. Derive voltage gain of non-inverting op-amp configuration. [2+4]
9. Design the summer circuit using operational amplifier: [5]  

$$V_0 = V_1 + 2V_2 + 3V_3$$
10. Explain the concept of gain stability. Describe the working principal of square wave generator circuit using operational amplifier. [1+4]
11. Explain the complete block diagram of communication system. [4]
12. What is optical fiber? What are the advantages of optical fibers over traditional communication systems? [1+3]
13. Write short notes on: (Any Two) [2×4]
  - a) Strain gauge      b) Data logger      c) Digital multimeter
14. Convert the following: (Any Three) [3×2]
  - a)  $(10101.101)_2 = (?)_{10}$
  - b)  $(9001180)_{10} = (?)_{BCD}$
  - c)  $(2AB.5E)_{16} = (?)_8$
  - d)  $(34)_{10} - (12)_{10}$  using 1's complement method.
15. Simplify the expression using K-Map,  $F(x, y, z) = X'YZ + X'Y'Z + XYZ$  and realize it using logic gates. [6]
16. Explain the operation of JK flip-flop with necessary diagrams and characteristics table. [4]

\*\*\*