


TRIBHUVAN UNIVERSITY
INSTITUTE OF ENGINEERING
Examination Control Division
2075 Chaitra

Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


Subject: - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

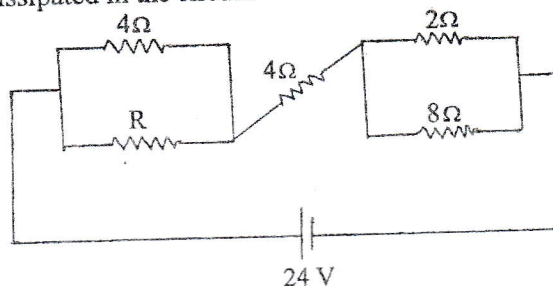
1. a) Discuss on brief voltage and current sources. Also justify the statement "terminal voltage goes on increasing on decreasing load current". [4]
- b) The resistance of the certain length of wire is 4.60 ohm at 20°C and 5.68 ohm at 80°C. Determine (i) the temperature coefficient of resistance of the wire at 0°C, (ii) the resistance of the wire at 60°C. [6]
- c) State and explain Kirchoff's current laws. Determine the value of unknown resistance R and the total current drawn from the source in the circuit of figure. Also compute the total power dissipated in the circuit. [6]



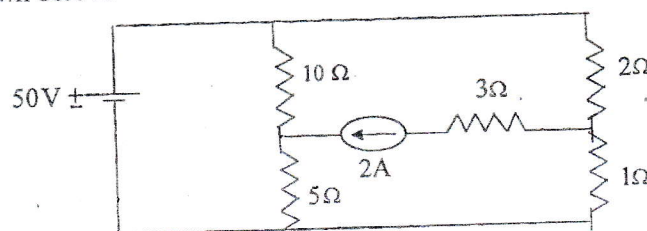2. a) Use loop current method to calculate the current through the 5 Ω resistance for the network shown below. [8]




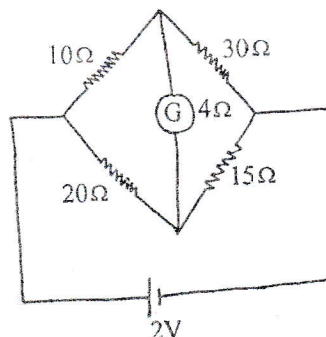- b) Using delta/star transformation, find the galvanometer current in the Wheatstone bridge. [8]




3. a) Find the current through R using thevenin's theorem. Also, find the value of R such that maximum power transfer takes place from the source to R in the network shown below.

[8]

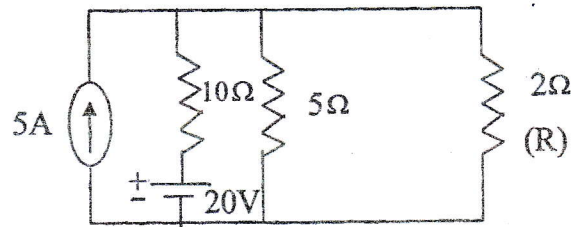

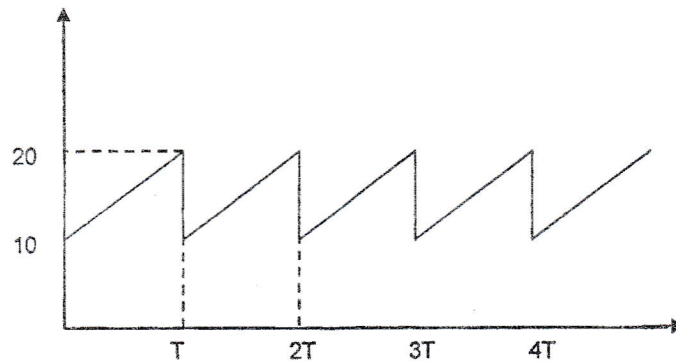- b) Derive an expression for the equivalent capacitance of a group of capacitors when they are connected in series. [4]
- c) Calculate the form factor and peak factor of the following waveform. [4]



4. a) State and explain Norton's theorem with a suitable example. [4]
- b) A resistance of $12\ \Omega$, an inductance of $0.15\ \text{H}$ and a capacitance of $130\ \mu\text{F}$ are connected in series across a 100V , 50Hz supply. Calculate the impedance, current and phase angle and power factor. [4]
- c) A parallel circuit consists of two branches, one containing a coil of resistance $5\ \Omega$ and inductance 38.2mH , the other a non-inductive resistance $16\ \Omega$ in series with a capacitor of $300\ \mu\text{F}$ capacitance. The circuit is connected to a $240\ \text{V}$, $50\ \text{Hz}$ supply. Determine (i) the current in each branch (ii) the total current (iii) the circuit phase angle (iv) the circuit impedance (e) the components of an equivalent circuit consisting of a resistance and reactance. [8]
5. a) Define power factor and explain causes of low factor. A single phase 240V , $50\ \text{Hz}$ induction motor takes 20A at power factor of 0.75 lagging. It is desired to raise the power factor to 0.95 lagging by connecting a capacitor across the load. Calculate the capacitance of the capacitor to be used in parallel with induction motor. [2+6]
- b) A three phase $400\ \text{V}$, $50\ \text{Hz}$ power line has two loads connected to it. The first is delta-connected and draws $25\ \text{Kw}$ at 0.70 power factor lagging. The second is wye-connected and draws $6.25\ \text{kVA}$ at 0.8 power factor leading. What is the total line current and the combined power factor. [8]
