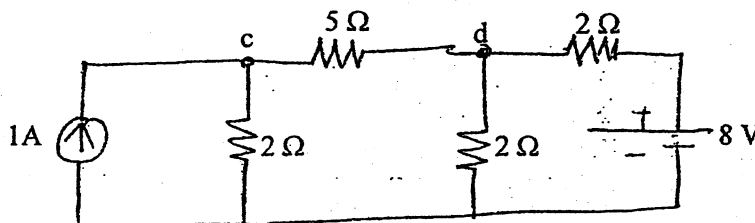


Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agric.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


Subject: - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) Explain ideal current and voltage sources. [4]
- b) Define temperature coefficient of resistance. The resistance of a certain length of wire is 4.6Ω at 20°C and 5.88Ω at 80°C . Determine (a) The temperature coefficient of resistance of the wire at 0° (b) The resistance of the wire at 60°C . [8]
- c) State and explain Superposition theorem with an appropriate example. [4]
2. a) Find out the current through 5 ohm resistor connected across the terminal c and d in the network shown below using the Venin's theorem. [8]



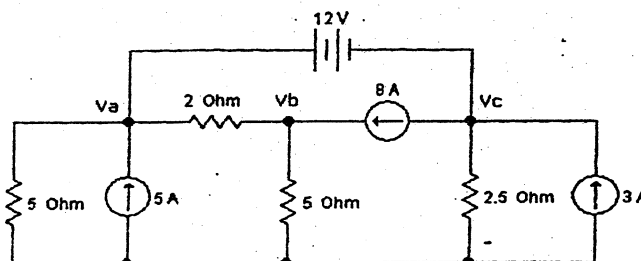
- b) Use Nodal Analysis Method to determine the V_a , V_b and V_c and calculate current through 2.5Ω . [8]



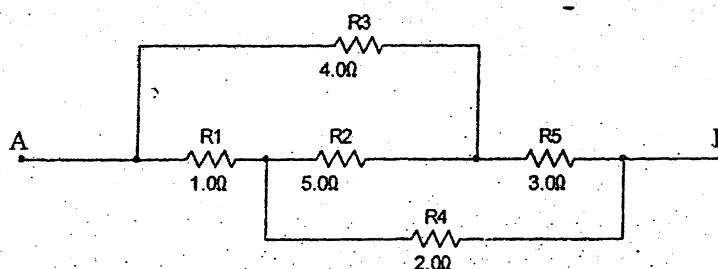
3. a) Find the resistance between the terminals A and B in the circuit segment below. [4]



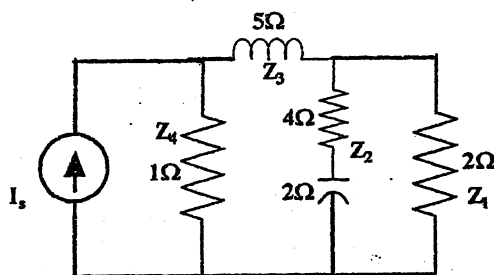- b) Three capacitors A, B and C have capacitances 10, 50 and 25 μF respectively. Calculate: [6]
- Charge on each when connected in parallel to a 250 V supply
 - Total capacitance and
 - p.d. across each when connected in series
- c) State Maximum Power Transfer Theorem and also prove "maximum power will be dissipated when $R_{\text{internal}} = R_L$ " [6]
4. a) Derive the expression for electrical current in a pure inductive circuit when input power is $V_m \sin \omega t$. Draw the wave form of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power. [6]
- b) In the given circuit, find the current through the inductor, what is the equivalent impedance? [6]



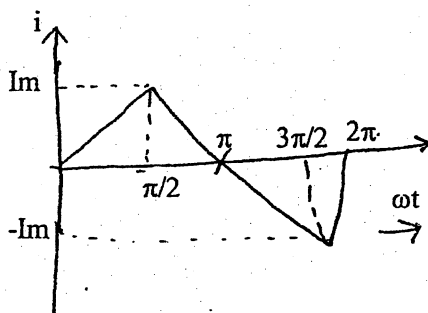- c) Find the peak factor and form factor of the triangular wave shown in figure below. [4]



5. a) Explain the importance of power factor in an ac circuit, with suitable example. How power factor can be improved? [4]
- b) A three phase star connected system with line voltage 400 V is connected to three loads: $25 \angle 0^\circ$, $11 \angle -20^\circ$ and $15 \angle 10^\circ$ (also connected in star). Find the line to line current, total power and current in the neutral of the system. [8]
- c) Define phase sequence and explain its significance in three phase system. [4]
