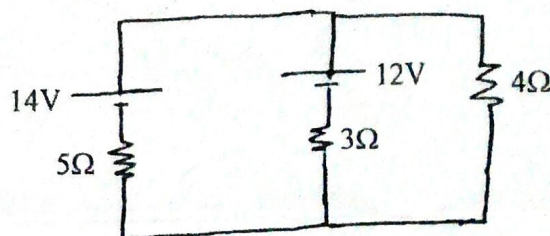


Exam.	Regular		
Level	BE	Full Marks	80
Programme	All (Except B.Arch.)	Pass Marks	32
Year / Part	I / II	Time	3 hrs.

Subject: - Basic Electronics Engineering (EX451)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt **All** questions.
- ✓ The figures in the margin indicate **Full Marks**.
- ✓ Assume suitable data if necessary.

1. State superposition theorem. In the following figure find the current flow in 4 ohm resistor using superposition theorem. [2+4]



2. Explain the principle of operation of RC low pass filter with necessary diagrams and derivation. [4]
3. Explain the working principle of full wave bridge rectifier circuit with the help of necessary circuit diagrams and expressions. [6]
4. Determine V_L , I_L , I_Z and I_R for the network shown in figure below for following condition. [3+3]

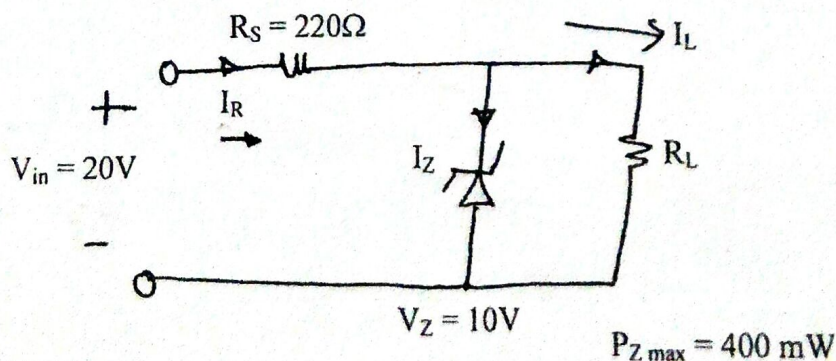- a) If $R_L = 180 \Omega$
b) If $R_L = 470 \Omega$



5. Define DC load line? Explain the common emitter configuration circuit with the help of input and output characteristics curve. [2+4]
6. Explain the construction and working principle of MOSFET. [6]
7. Write the four properties of ideal operational amplifier. [2+4]
8. Explain how square wave can be generated using Op-Amp. [6]

9. Define communication system. Explain amplitude modulation communication system with the help of necessary block diagrams. [6]
10. Discuss the role of antenna in communication system. What are the advantages and disadvantages of optical fiber communication? [2+4]
11. Draw the circuit of X-OR gate using NAND gates only. Perform the subtraction using 2's complement method. [2+2]
- 42₍₁₀₎ - 115₍₁₀₎ [4]
12. Simplify the expression using k-map [4]
- $$F(x, y, z) = xyz + x'y'z + xy'z' + x'y'z' + x'yz$$
13. Discuss the operation of S-R flip flop. [5×2]
14. Write short notes: (any two)
- a) Clipper circuit
 - b) Strain gauge transducer
 - c) Data logger
