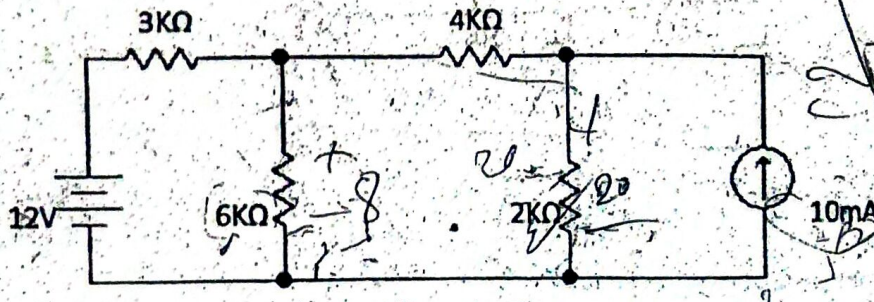


Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	All (Except B.Arch.)	Pass Marks	32
Year / Part	I / II	Time	3 hrs.

**Subject: - Basic Electronics Engineering**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. State Thevenin's theorem and use it to find the current through  $4K\Omega$  resistor. [2+6]



2. Explain large signal model of PN junction diode. [6] (6)
3. Explain the working principle of half wave rectifier with necessary diagrams. [6] (5)
4. Explain any two DC-biasing methods of BJT with necessary derivations and diagrams. [8]
5. Why BJT is bipolar and MOSFET is a unipolar device? Draw the circuit diagram of NOT gate using CMOS. [2+2]
6. Mention any five properties of IDEAL Op-Amp. Draw the circuit diagram and explain the operation of square wave generator using Op-Amp. [2+4]
7. Find the voltage gain of non inverting Op-Amp. (3) [4]
8. Briefly describe about the block diagram of communication system. (4) [5]
9. What do you mean by electromagnetic waves? How are they propagated? Explain. (3) [2+3]
10. Simplify the expression using K-Map,  $F(A, B, C) = A'B + BC' + AC'$ . [3]
11. What is multiplexer (MUX)? Explain 4:1 multiplexer. [3]
12. Perform the followings: [1.5×4]
- $(903)_{10} = (?)_{BCD}$
  - $(624.03)_8 = (?)_{16}$
  - $(101101)_2 + (10111)_2 = ?$
  - Subtract using 2's complement:  $(14)_{10} - (11)_{10}$
13. Write short notes on: (any four). [4×4]
- Regulated Power Supply
  - Application circuit of strain gauge
  - Comparison of digital and analog instruments
  - Data logger
  - Light Emitting Diode (LED)
  - Diode Clamper Circuit