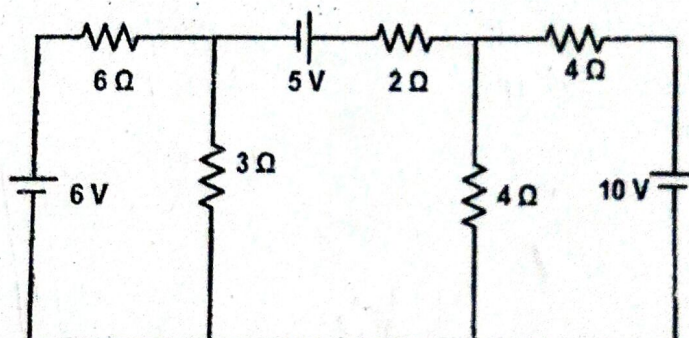


Exam.	Back		
Level	BE	Full Marks	80
Programme	BCE, BGE, BME	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) Derive a relation between the known resistance  $R_1$  at  $t_1$  °C and the unknown resistance  $R_2$  at  $t_2$  °C, when  $\alpha_0$  is not known. [6]
- b) Explain the process of source conversion. How is it helpful in solving electrical networks? [4]
- c) A circuit, containing of three resistances  $12\ \Omega$ ,  $18\ \Omega$ , and  $36\ \Omega$  respectively jointed in parallel, is connected in series with a fourth resistance. The whole is supplied at  $60\text{ V}$  and it is found that the power dissipated in the  $12\ \Omega$  resistance is  $36\text{ W}$ . Determine the value of the fourth resistance and the total power dissipated in the group. [6]
2. a) Find the branch currents in the circuit of given figure below by using nodal analysis? [6]



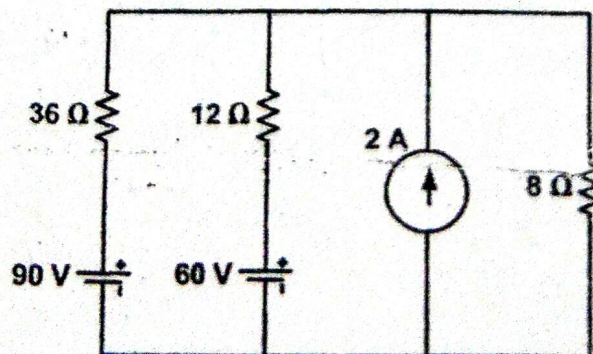
- b) Find current in  $8\ \Omega$  resistor of the network shown in figure below using superposition theorem. [6]



- c) State and explain Thevenin's theorem with suitable example. [4]



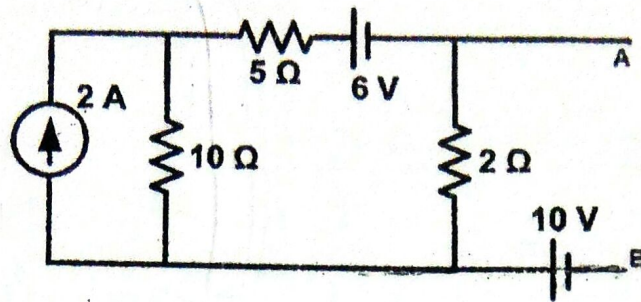3. a) In the network shown in figure below, find resistance  $R_L$  connected between terminals A and B so that maximum power is develop across  $R_L$ . What is the maximum power? [6]



- b) Derive an expression for the energy stored in the magnetic field of an inductor. [4]
- c) Derive an expression for the current drawn by a pure capacitor when connected across a voltage. Explain with the help of a power diagram that the value of average power drawn by the capacitor during one cycle is zero. [6]
4. a) A resistance of  $20\ \Omega$ , an inductance of  $0.2\ \text{H}$  and a capacitance of  $100\ \mu\text{F}$  are connected in series across a  $220\ \text{V}$ ,  $50\ \text{Hz}$  supply. Determine the following (a) impedance (b) Current (c) Voltage across R, L and C and (d) Power factor. Also calculate the total power consumed by the circuit. [6]
- b) A coil resistance  $50\ \Omega$  and inductance  $0.318\ \text{H}$  is connected in parallel with a circuit comprising a  $75\ \Omega$  resistor in series with a  $159\ \mu\text{F}$  capacitor. The resulting circuit is connected to a  $240\ \text{V}$ ,  $50\ \text{Hz}$  ac supply. Calculate: (a) The supply current (b) The circuit impedance, resistance and reactance (c) Power factor and (d) Total power consumed by the circuit. [6]
- c) Describe the method of measuring power in 3- $\Phi$  circuit by using two watt meters. [4]
5. a) A  $220\ \text{V}$ ,  $50\ \text{Hz}$  single phase ac motor draws a power of  $10\ \text{kW}$  at a power factor of  $0.75$  lagging. Calculate the change in current taken from the supply and the new power factor when a  $250\ \mu\text{F}$  capacitor is connected in parallel with the motor. If the motor is supplied through a cable of  $0.05\ \Omega$  resistances, calculate the power loss in the cable before and after connecting the capacitor. [8]
- b) A three-phase  $\Delta$ -connected load consists of three similar coils, each of resistance  $50\ \Omega$  and inductance  $0.3\ \text{H}$ . The supply is  $415\ \text{V}$ ,  $50\ \text{Hz}$ . Calculate (i) The line currents (ii) The power factor (iii) Total active and reactive powers when the load is  $\Delta$ -connected. Draw the phasor diagram. [8]

\*\*\*