

38


04 TRIBHUVAN UNIVERSITY
INSTITUTE OF ENGINEERING
Examination Control Division
2070 Magh

New Back (2066 & Later Batch)			
Exam.	BE	Full Marks	80
Level	All (Except B.Arch)	Pass Marks	32
Programme	I / II	Time	3 hrs.

Subject: - Basic Electronics Engineering (EX451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

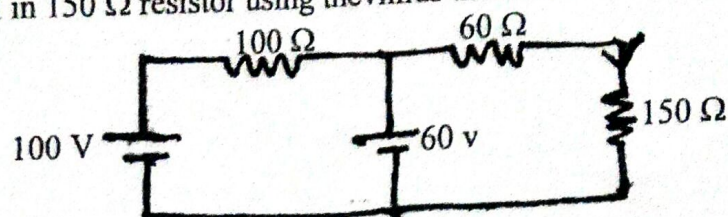1. Find the current I in $150\ \Omega$ resistor using thevenius theorem. [6]




2. Find the value of resistor from following colour code. [2]

a) Red Orange Green Silver b) Yellow Black Gold Gold


3. Explain the operation of RC high pass filter circuit with the help of necessary diagrams and figures. [4]

4. Describe IV characteristics of PN Junction diode. [6]

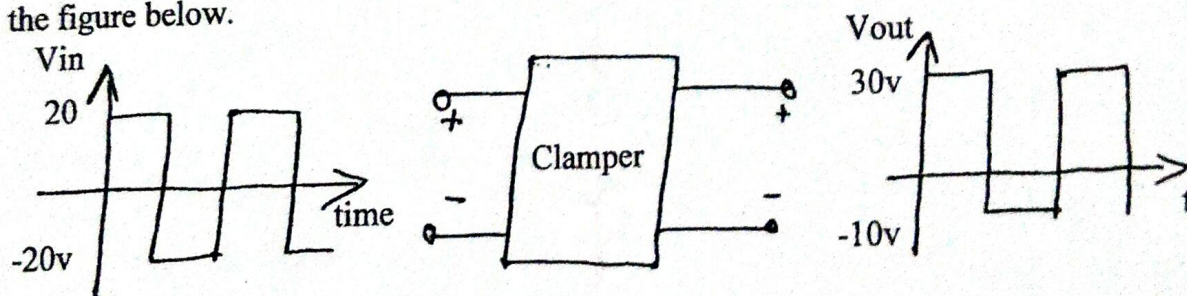5. What is a clamper circuit? Design a clamper circuit to perform the function indicated in the figure below. [2+4]



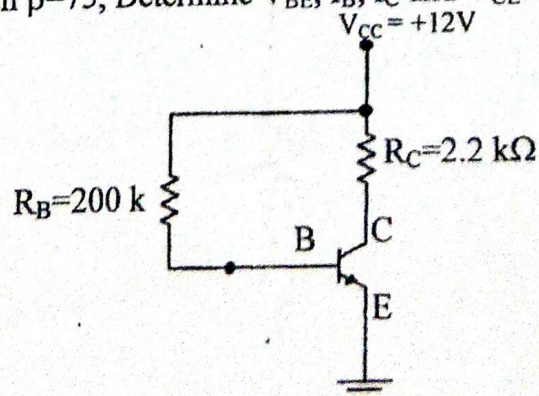6. For the given circuit with $\beta=75$, Determine V_{BE} , I_B , I_C and V_{CE} . [6]



7. Explain how BJT can be used as a switch. What are the difference between MOSFET and BJT? [4+2]

8. Explain the concept of virtual ground in op-amp. Design a summer circuit using op-amp to get the output voltage as: $V_0 = -(V_1 + 10V_2 + 25V_3)$ [2+4]
9. How do you define positive feedback? Draw the circuit for Wein bridge oscillator and explain the principle of operation. [2+4]
10. What are the advantages of optical fiber communication system? Draw and label the diagram of optical fiber. [3+3]
11. Explain why modulation is needed in Communication System. Mention any three parameters of antenna. [3+3]
12. Simplify the given function using K-map method. $F(A, B, C) = \Sigma (0, 1, 2, 5) + D (3, 4, 6)$ and implement the simplified circuit using NAND only. [3+3]
13. What is the difference between combinational and sequential circuit. Discuss JK flip-flop with the help of logic diagram. [2+6]
14. Write short notes on: (any two) [3×2]
- a) Data logger
 - b) Regulated power supply
 - c) Digital Multi-meter
