


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B.Agric.	Pass Marks	32
Year / Part	1 / I	Time	3 hrs.

Subject: - Basic Electrical Engineering (EE401)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) A 60 W, 240 V incandescent filament lamp is switched on at 20°C. The operating temperature of the filament is 2000°C. Determine the current taken by the lamp at the instant of switching ON. the temperature coefficient of resistance of the filament material is 0.0045/K. [6]

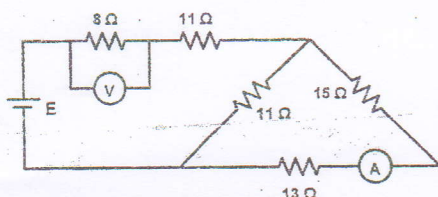
- b) A battery of unknown emf is connected across resistances, as shown in figure below. The voltage drops across the 8 Ω resistor is 20 V. What will be the current reading in the ammeter? What is the emf of the battery? [5]



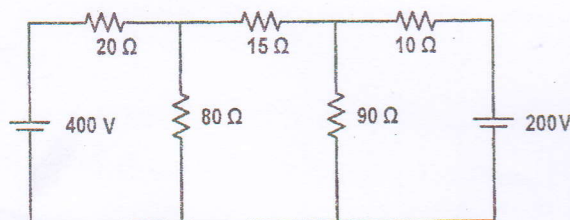- c) What do you mean by ideal and practical voltage and current sources? [5]
2. a) Find the power dissipation in 15 Ω resistor shown in figure below using mesh analysis. [6]



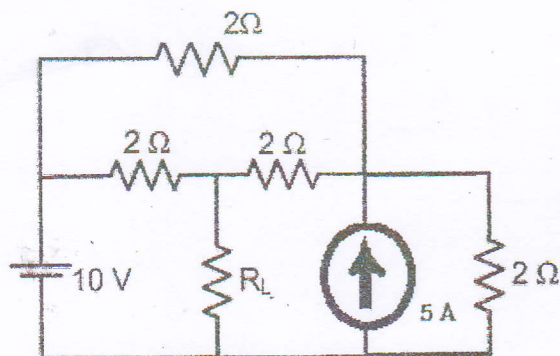
- b) Find current on load resistor R_L , if its resistance is 2 Ω, using superposition theorem. [6]



- c) State and explain Norton's theorem with an appropriate example. [4]

3. a) Find the value of R_L for which the maximum power is transferred in the load resistance R_L . Also find the maximum power that can be transferred to the load resistance R_L .

[8]

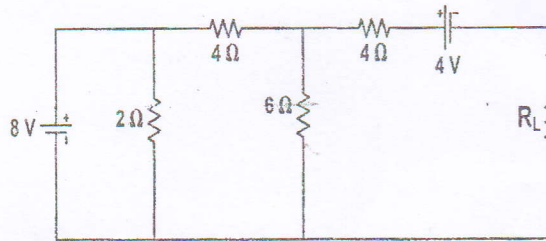


- b) Derive the expression for the inductance of inductor in terms of its physical dimensions.

[4]

- c) Calculate the average and rms value of full-wave rectified sine wave as shown below.

[4]

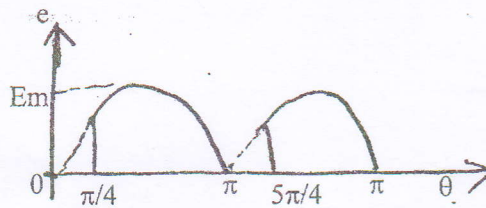

4. a) A circuit consisting of a resistance of $30\ \Omega$ in series with an inductance of 75 mH is connected in parallel with a circuit consisting of a resistance of $20\ \Omega$ in series with a capacitance of $100\ \mu\text{F}$. If the parallel combination is connected to a 240 V , 50 Hz single phase supply, calculate (i) The current in each branch (ii) The total current and power factor and (iii) Power consumed. Also draw a neat phasor diagram.

[8]

- b) For a series path with a resistance of $8\ \Omega$, capacitor of $120\ \mu\text{F}$ and an inductance of 0.1 H , a capacitor $180\ \mu\text{F}$ is kept in parallel. Then the combination is fed by 240 V , 50 Hz , $1\text{-}\phi$ supply. Calculate branch currents, total current from supply, power factor of whole circuit, active power and reactive power consumed by the circuit. Also show phasor diagram.


[8]

5. a) Develop relation between phase voltage and line voltage in $3\text{-}\phi$ star connected system.

[4]

- b) For the circuit shown in figure below, calculate the current through the neutral and the total power consumed in the load.

[8]

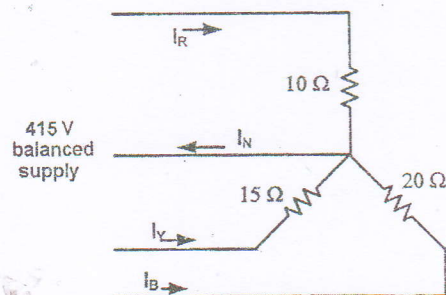

- c) Explain with connection diagram the measurement of $3\text{-}\phi$ power using two wattmeters.

[4]
