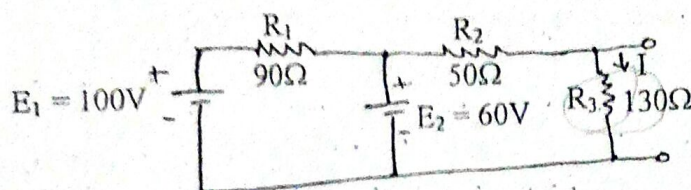


Exam. Level	BE	Regular / Back	
		Full Marks	80
Programme	All (Except B. Arch)	Pass Marks	32
Year / Part	I / II	Time	3 hrs.

Subject: - Basic Electronics Engineering

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) Describe the principle of Thevenins theorem by solving following problem. [7]



Find the current I in R_3 .

- b) Draw the circuit diagram of RC low filter and explain its operation with the help of frequency dependent output waveform. [7]
2. a) Draw and explain the I-V characteristics curve of P-N junction diode for forward and reverse bias region. [7]
- b) Draw Zener voltage regulator circuit and explain clearly the working principle of this circuit to produce a regulated dc output. [7]
3. a) Describe output characteristics of common emitter configuration with the help of circuit diagram and IV characteristics graph. [7]
- b) Describe the construction and working principle of N Channel E-MOSFET. [7]
4. a) State four important properties of ideal op-amp. Draw the circuit diagram of differentiating amplifier using op-amp and derive the expression for V_{out} . [2+5]
- b) i) Draw the circuit diagram of Wien Bridge oscillator circuit for sinusoidal wave form. [4+3]
- ii) Draw square wave oscillator circuit.
5. a) Perform the conversion of the following: [6]
- i) $(10111.101)_2 = (?)_{10}$
- ii) $(AFC.00)_{16} = (?)_8$
- iii) $(901)_{10} = (?)_{BCD}$
- b) Simplify the expressions and draw the circuits [6]
- i) $\bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + A \bar{B} \bar{C} + A \bar{B} C$
- ii) $A \bar{C} + ABC + A(C + \bar{A}C)$
6. Write short notes on any two: [2×6]
- a) Strain Gauge
- b) $\lambda/2$ Dipole Antenna
- c) Transducer
- d) Amplitude Modulation (AM)