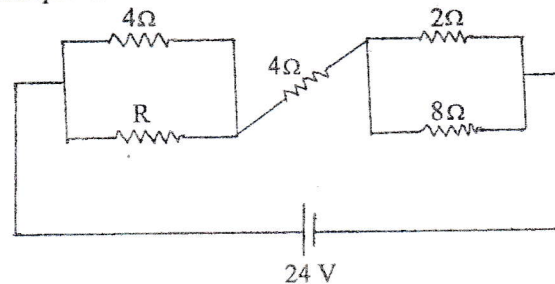


Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) Discuss on brief voltage and current sources. Also justify the statement "terminal voltage goes on increasing on decreasing load current". [4]
- b) The resistance of the certain length of wire is 4.60 ohm at 20°C and 5.68 ohm at 80°C. Determine (i) the temperature coefficient of resistance of the wire at 0°C, (ii) the resistance of the wire at 60°C. [6]
- c) State and explain Kirchoff's current laws. Determine the value of unknown resistance R and the total current drawn from the source in the circuit of figure. Also compute the total power dissipated in the circuit. [6]



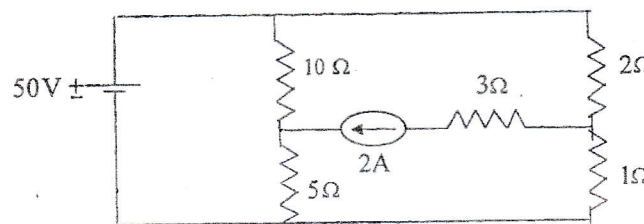2. a) Use loop current method to calculate the current through the 5 Ω resistance for the network shown below. [8]




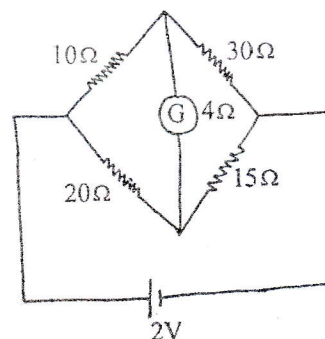- b) Using delta/star transformation, find the galvanometer current in the Wheatstone bridge. [8]



3. a) Find the current through R using thevenin's theorem. Also, find the value of R such that maximum power transfer takes place from the source to R in the network shown below.


[8]

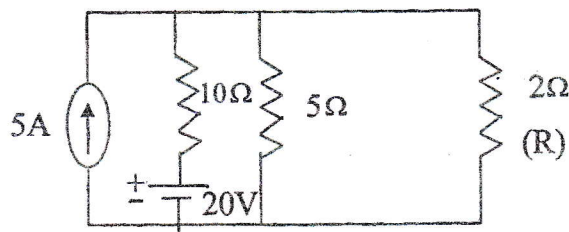

- b) Derive an expression for the equivalent capacitance of a group of capacitors when they are connected in series.
- c) Calculate the form factor and peak factor of the following waveform.

[4]

[4]

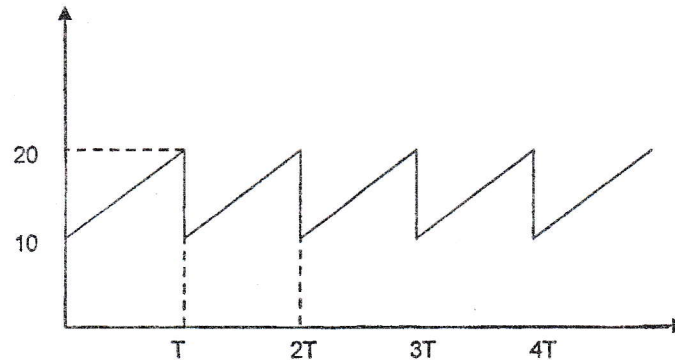

4. a) State and explain Norton's theorem with a suitable example.
- b) A resistance of  $12\ \Omega$ , an inductance of  $0.15\ \text{H}$  and a capacitance of  $130\ \mu\text{F}$  are connected in series across a  $100\text{V}$ ,  $50\text{Hz}$  supply. Calculate the impedance, current and phase angle and power factor.
- c) A parallel circuit consists of two branches, one containing a coil of resistances  $5\ \Omega$  and inductance  $38.2\text{mH}$ , the other a non-inductive resistance  $16\ \Omega$  in series with a capacitor of  $300\ \mu\text{F}$  capacitance. The circuit is connected to a  $240\ \text{V}$ ,  $50\ \text{Hz}$  supply. Determine (i) the current in each branch (ii) the total current (iii) the circuit phase angle (iv) the circuit impedance (e) the components of an equivalent circuit consisting of a resistance and reactance.
5. a) Define power factor and explain causes of low factor. A single phase  $240\text{V}$ ,  $50\ \text{Hz}$  induction motor takes  $20\text{A}$  at power factor of  $0.75$  lagging. It is desired to raise the power factor to  $0.95$  lagging by connecting a capacitor across the load. Calculate the capacitance of the capacitor to be used in parallel with induction motor.
- b) A three phase  $400\ \text{V}$ ,  $50\ \text{Hz}$  power line has two loads connected to it. The first is delta-connected and draws  $25\ \text{Kw}$  at  $0.70$  power factor lagging. The second is wye-connected and draws  $6.25\ \text{kVA}$  at  $0.8$  power factor leading. What is the total line current and the combined power factor.

[4]

[4]

[8]

[2+6]

[8]

\*\*\*