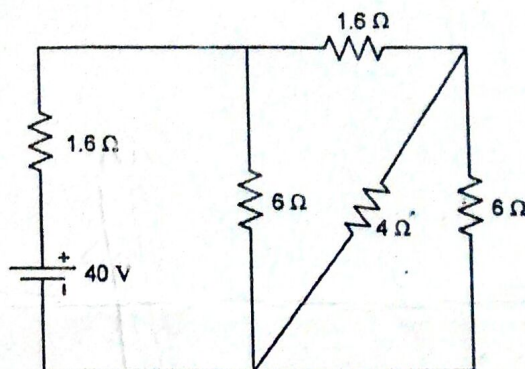


Exam.	BE	Regular	
Level	BE	Full Marks	80
Programme	BCE, BME	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


Subject: - Basic Electrical Engineering

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any Five questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) What do you mean by ideal and practical voltage source? Explain the effect of an internal resistance of a voltage source on its terminal characteristics. [2+3]
- b) The coil of a relay takes a current of 0.12A when it is at the room temperature of 15°C and connected across a 60-V supply. If the minimum operating current of the relay is 0.1A, calculate the temperature above which the relay will fail to operate when connected to the same supply. Resistance-temperature coefficient of the coil material is 0.0043 per °C at 6°C. [6]
- c) Find the current through 4Ω resistance. [5]



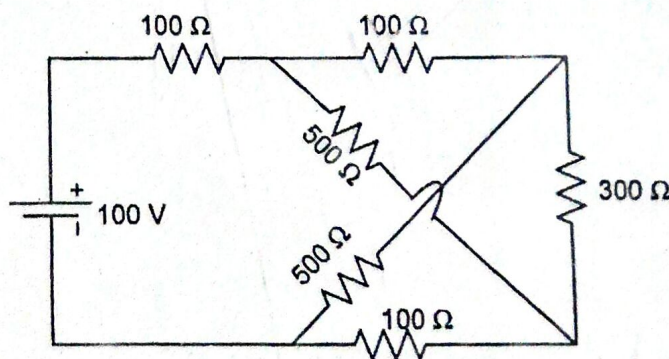2. a) State and explain Kirchoff's laws. Determine the current supplied by the battery in the circuit shown in figure below. [2+4]




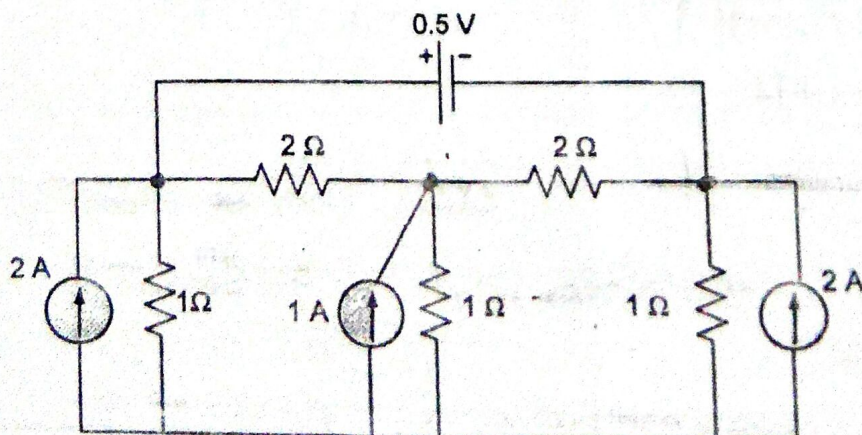- b) Obtain the voltages at each nodes by applying nodal voltage analysis. [6]




- c) State and explain Norton's theorem with an appropriate example. [4]

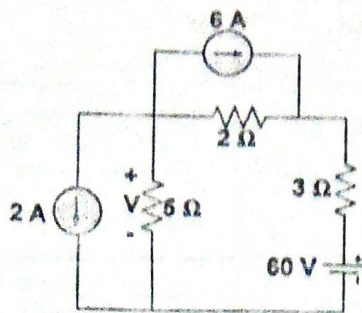3. a) State superposition theorem. Apply superposition theorem to the circuit shown below to find the voltage drop V across the 5Ω resistor. [8]




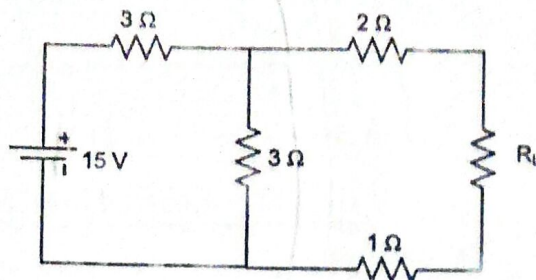- b) Find the value of R_L such that maximum power will be transferred to R_L . Find the value of the maximum power. [8]



4. a) Derive the equation for instantaneous current flowing through a pure capacitor when excited by AC sinusoidal voltage $v = V_m \sin \omega t$. Draw the waveform of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power. [4]

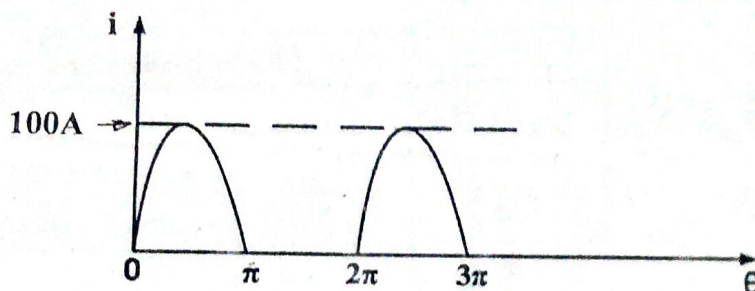- b) Calculate the RMS and average values of the rectified sine wave of 50Hz. [6]



- c) Two coils A and B are connected in series across a 240V, 50Hz supply. The resistance of A is 5Ω and the inductance of B is 0.015H. If the input from the supply is 3 kW and 2 kVAR, find the inductance of A and the resistance of B. Calculate the voltage across each coil. [6]
5. a) Two impedances consists of (resistance of 15Ω and series connected inductance of 0.04H) and (resistance of 10Ω , inductance of 0.1 H and a capacitance of $100\mu\text{F}$, all in series) are connected in series and are connected to a 230V, 50Hz a.c. source. Find: (i) current drawn, (ii) voltage across each impedance, (iii) total power factor and (iv) draw the phasor diagram. [6]
- b) What are the two ways of connecting a 3-phase system? Draw their phasor diagrams and write down the relationship between phase and line voltages and currents for these systems. [4]
- c) Define power factor and explain the disadvantages and causes of low power factor? [6]
6. a) List out the advantages of 3 phase system over single phase system. [4]
- b) Explain 2-wattmeter method for the measurement of power in a balanced three phase load. How are the readings of the two wattmeters affected, when the load power factors is very low. [6]
- c) A 220V, 3-phase voltage is applied to balanced delta connected 3-phase load of phase impedance $(15 + j20)\Omega$. Calculate: [6]
- The phase voltages
 - The power current in each line
 - The power consumed per phase
 - Draw the phasor diagram
 - What is the phasor sum of three line currents? Why does it have this value?