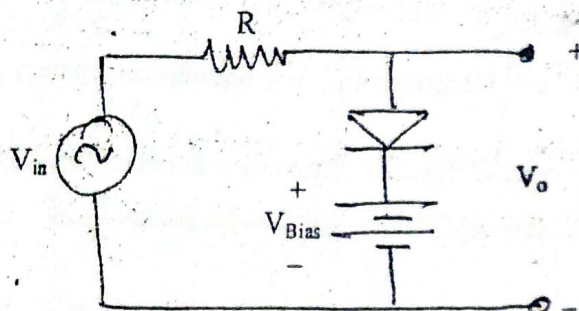


Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	All Except (B.Arch.)	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


*Subject: - Basic Electronics Engineering (EX451)*

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. What do you mean by filter? Explain the RC low pass and high pass filter with corresponding transfer function and magnitude. [1+4]
2. State Thevenin's Theorem. Write down the steps for determining  $V_{th}$  and  $R_{th}$  with necessary circuit diagrams. [1+4]
3. What is rectification? Explain the operation of half wave rectifier with necessary diagrams. [1+4]
4. What are clippers? Draw the sinusoidal waveform of the following circuit and indicate the output voltage. Assume diode is ideal. [1+4]



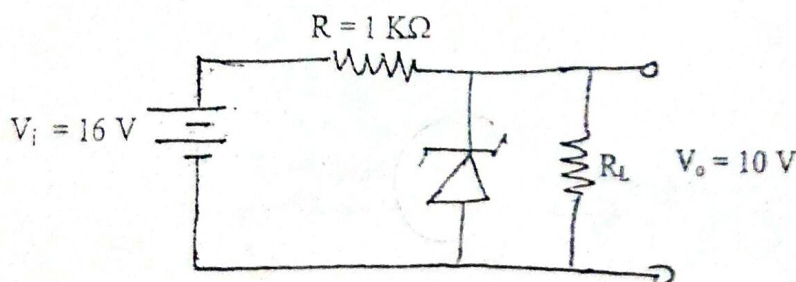5. Find the zener current from the given zener diode network when  $R_L = 3 \text{ K}\Omega$  and  $V_o = 10 \text{ V}$ . [5]



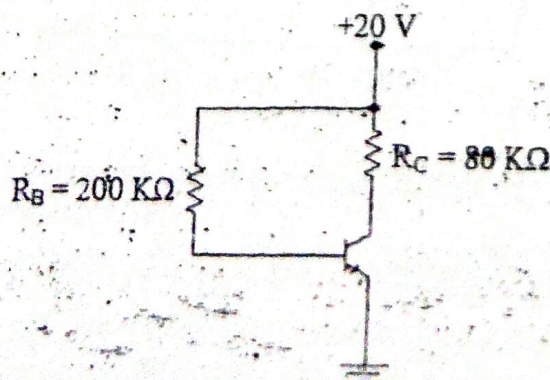6. For the given circuit with  $\beta = 75$ , determine  $I_B$ ,  $I_C$  and  $V_{CE}$ . [2+2+2]





7. Explain the construction and working principle of enhancement type MOSFET? [6]
8. Explain the concept of feedback theory. Describe the working principal of square wave oscillator circuit using op-amp. [2+4]
9. State any 4 important properties of ideal Op-Amp. Draw the circuit diagram of differentiator using Op-Amp and show that output is the differentiation of input signal. [2+4]
10. What is modulation? Explain AM and FM modulated wave. [1+2+2]
11. What do you mean by electromagnetic waves? How are they propagated? Explain. [2+3]
12. Perform the following: [4×1]
  - a)  $(375.37)_8 = (?)_{16}$
  - b)  $(169.03125)_{10} = (?)_2$
  - c)  $(905)_{10} = (?)_{BCD}$
  - d) Subtract  $(25)_{10}$  from  $(49)_{10}$  using 2'S complement method
13. Simplify the following Boolean expression using K-map and realize it by using universal gate of your interest. [3+2]
 
$$F(x, y, z) = xy + \bar{x}z + yz$$
14. Explain SR flip-flop with circuit. [4]
15. What is instrumentation system? Describe the instrumentation system with block diagram. [4]
16. Explain briefly about remote control or digital multimeter with necessary diagrams. [4]

\*\*\*