

TRIBHUVAN UNIVERSITY
INSTITUTE OF ENGINEERING
Examination Control Division
2076 Chaitra

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEI	Pass Marks	32
Year / Part	I / I	Time	3 hrs.

Subject: - Digital Logic (EX 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. Write the basic difference between analysis and digital signals with examples. [3]
2. Perform the following code conversions. [1.5×4]
 - (i) $(430.25)_8 = (?)_{16}$
 - (ii) $(39.75)_{10} = (?)_8$
 - (iii) $(17)_{10} = (?)_{\text{gray}}$
 - (iv) $(17)_{\text{excess-3}} = (?)_{\text{BCD}}$
3. a) State and prove De-Morgan's laws. [2]
 b) Realize 3 inputs XOR gates using NAND gates only. [3]
4. Define minterms and maxterms. Simplify the following using k-map and implement the result using NOR gates only. [2+4+2]

$$F(A,B,C,D) = \sum m(0,1,2,5,8,14) + d(4,10,13)$$
5. Implement 1:16 demultiplexer using 1:2 demultiplexer. [4]
6. What is hazard? Explain types of hazards with hazard cover techniques used in K-map simplification. [1+4]
7. Define excess-3 code with examp. Design a binary to excess-3 code converter circuit using basic gates. [2+5]
8. Differentiate between combinational and sequential circuit. Explain working principle of master slave JK flip-flop. [2+4]
9. Define shift registers with its application. Explain the working principle of 4 bit Ring counter with its timing diagram. [2+5]
10. Design a 3 bit synchronous up counter where the bit combination of each states are in gray system. (Use T-flip-flop in your design.) [8]
11. Using mela circuit with J-K flip-flops design a synchronous sequence detector that produces output $Z=1$ when it detects the serial input $X=010$. [10]
12. Differentiate between RAM and ROM. Implement $F1 = \sum(1,2,4,6)$ and $F2 = \sum m(0,2,3)$ using PROM. [2+4]
13. What are the applications of digital devices? Explain frequency counter. [1+4]
