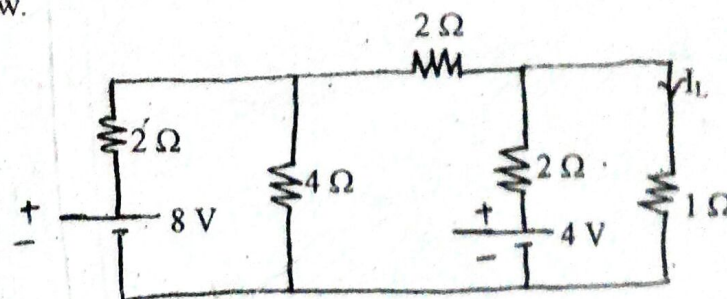


Exam.	New Batch (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BCE, BME, BOE	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


Subject: - Basic Electrical Engineering (EE451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) At room temperature of 20°C , the current flowing at the instant of switching of a 40W filament lamp with 220V supply is 2A. The filament material has a resistance temperature coefficient of $0.005/^{\circ}\text{C}$ at 20°C . Calculate the working temperature of filament and current taken by it during normal working condition. [6]
- b) Derive the formula $I = n.A.e.V$ where the symbols used have their usual meaning. [5]
- c) Apply KVL and KCL to determine current I_L through 1Ω resistor in the network shown below. [5]



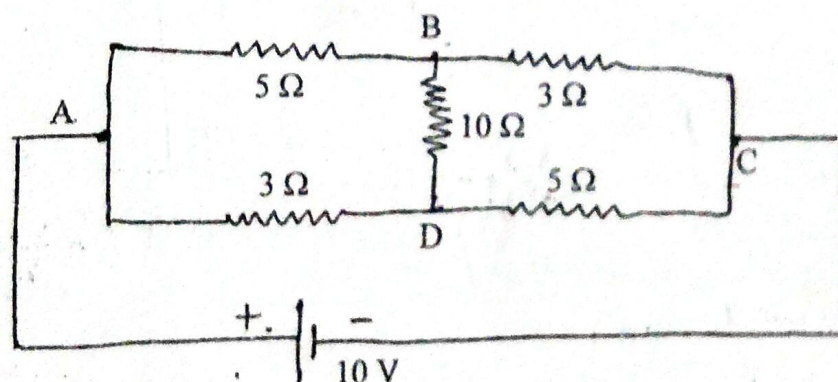
2. a) Define maximum power transfer theorem and derive the condition for maximum power transfer across the load resistance. [8]
- b) Find the current in the branch BD of the circuit given below by using Thevenin's. [8]



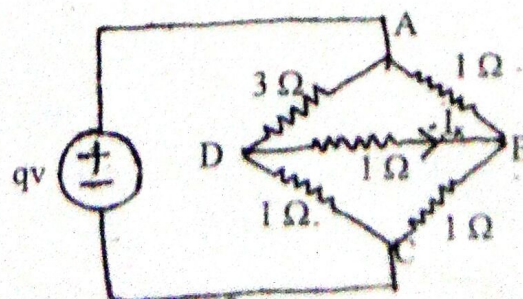3. a) Derive the equation for instantaneous current flowing through a pure inductor when excited by an ac sinusoidal voltage $v = v_m \sin \omega t$. Draw the wave form of voltage and current and also show analytically and graphically that it does not consume real power. [8]
- b) Find the value of I_x in the circuit shown below by the method of nodal analysis. [8]



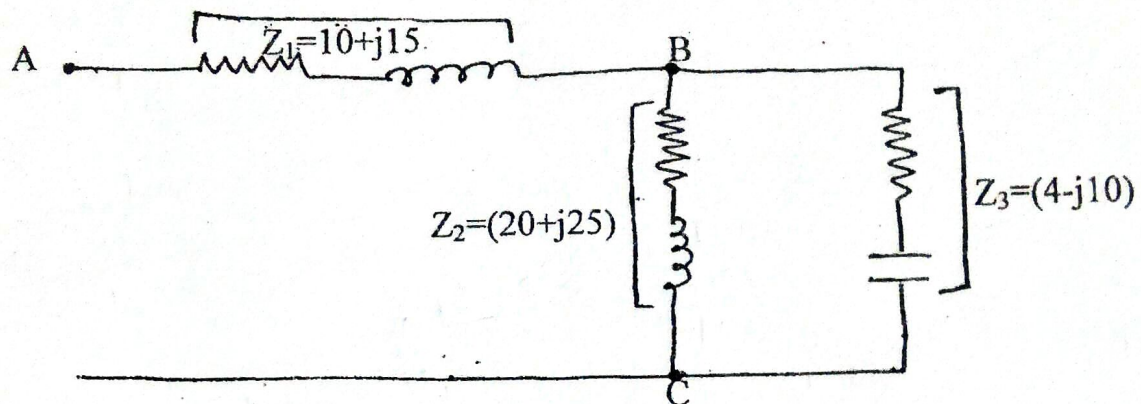4. a) What do you understand by dynamically and statically induced emfs? Hence define self and mutually induced emf and magnetic coupling between two coils. [4]
- b) Derive an expression for the equivalent inductance of two inductors when they are connected in series (i) adding combination (ii) Opposing combination [6]
- c) A $10\ \Omega$ resistor is connected in series with a $100\ \mu\text{F}$ capacitor to a $230\ \text{V}$, $50\ \text{Hz}$ supply. Find (i) The impedance (ii) Current (iii) Power factor (iv) Phase angle (v) Voltage across the resistor and the capacitor. [6]
5. a) Three elements, a resistance of $100\ \Omega$, an inductance of $0.1\ \text{H}$ and a capacitance of $150\ \mu\text{F}$ are connected in parallel to a $230\ \text{V}$, $50\ \text{Hz}$ supply. Calculate the : (i) Current in each element (ii) Supply current (iii) Phase angle between the supply voltage and the supply current with the help of a phasor diagram. [6]
- b) In the circuit shown in figure below, determine the equivalent impedance that appears across the terminals AC. [4]



- c) For the 3-phase delta connected circuit below. Determine the line currents and total active, reactive and apparent power. [6]

