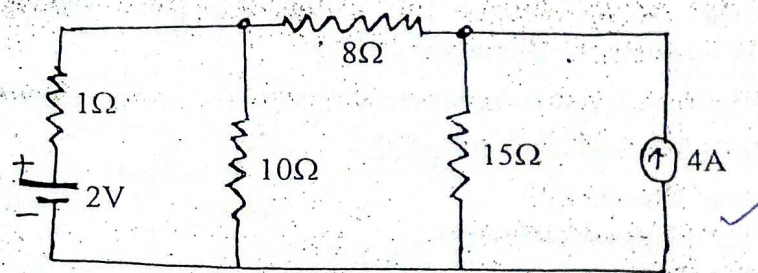


Exam.	New Back (2065 & Earlier Batch)		
Level	BE	Full Marks	80
Programme	BCE, BME	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


Subject: - Basic Electrical Engineering

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any Five questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) Describe the different types of energy sources for electricity generation. Which sources are more effective in the context of our country and why? [8]
- b) Explain electromotive force, potential difference and current with a circuit diagram. [3]
- c) State and explain Kirchoff's voltage law. [5]
2. a) State Superposition theorem and list the steps involved in applying it for the analysis of a resistor network with example. [8]
- b) Using Thevenin's theorem, find the current through 8Ω resistor in the circuit shown below. [8]



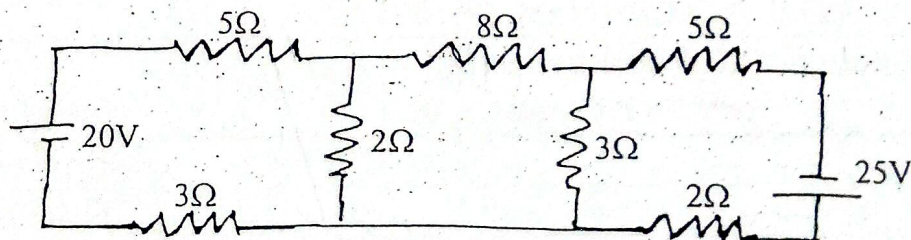3. a) Using nodal analysis find the current through 8Ω resistor. [8]



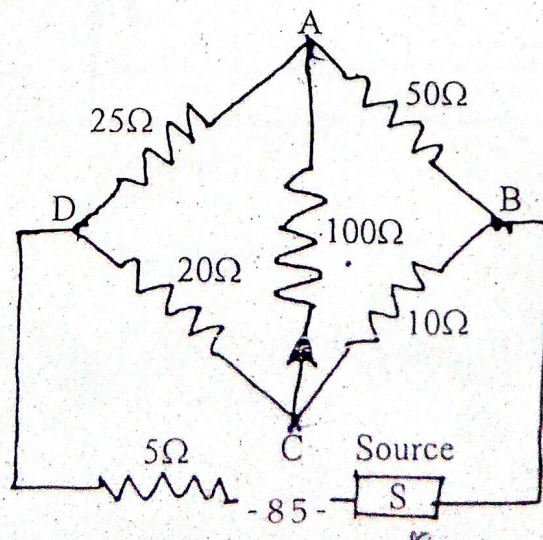- b) Use Kirchoff's law to determine the magnitude of current and polarity of the source if the current flowing through branch AC is $0.2A$ from C to A in the circuit shown below. [8]



4. a) Define capacitance and derive the equation for the charge stored in a capacitor. [4]
 b) The impressed voltage and the current flowing through a circuit are, [4]
 $v = 500 \sin(400t + \pi/3)$ and $i = 5 \sin(400t - \pi/6)$
 Determine:
 i) rms value of v & i
 ii) Phase difference
 iii) Power consumed in the circuit
- c) A 220V, 50Hz ac supply is applied to a coil of 0.07H and effective resistance 3.0Ω [8]
 connected in series with a $7.0 \mu\text{F}$ capacitor. Calculate
 i) Voltage across R, L and C
 ii) Current
 iii) Phase angle of the circuit
 iv) Draw the vector diagram
5. a) Define power and power factor. [4]
 b) Explain the importance of power factor in electricity generation with example. [4]
 c) Two impedances $Z_1 = (10 + j15)\Omega$ and $Z_2 = (6 - j8)\Omega$ are connected in parallel. Total [8]
 current supplied is 15A. Find: (i) Current in each branch (ii) Supply voltage and its
 phase angle w.r.t. the total current and (iii) Draw the phasor diagram.
6. a) Derive the relation between line voltage and phase voltage in a 3 - phase star [8]
 connected generator with phasor diagram.
 b) A 220V, 3 ϕ voltage is applied to a balanced delta connected 3 ϕ load of phase [8]
 impedance $(15 + j20)\Omega$. Find:
 i) Current in each line
 ii) Power consumed per phase
 iii) Power factor
