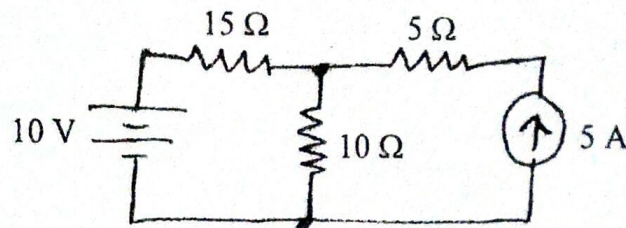


Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	All (Except B.Arch.)	Pass Marks	32
Year / Part	I / II	Time	3 hrs.



**Subject:** - Basic Electronics Engineering (EX451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


- Define active and passive circuit component. Determine the color code of the following resistor  $75 \text{ K}\Omega \pm 10\%$ . [2+2]
- Determine the current through  $10 \Omega$  resistance using Thevenin's theorem. [4]



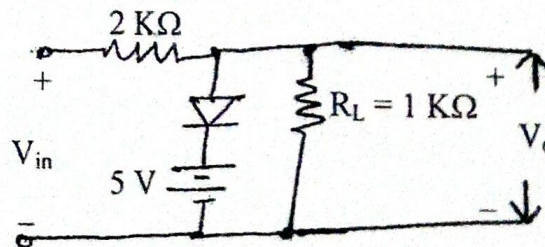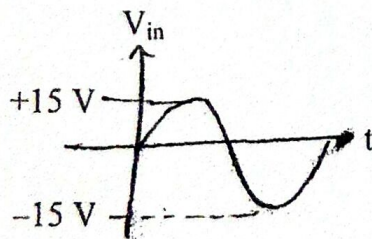- What is a filter? Explain the types of filter with necessary diagrams. [1+3]
- Explain large signal models of PN junction diode. [4]
- Define clipping circuits. Draw the output waveform of circuit shown below. Assume real silicon diode. [2+2]



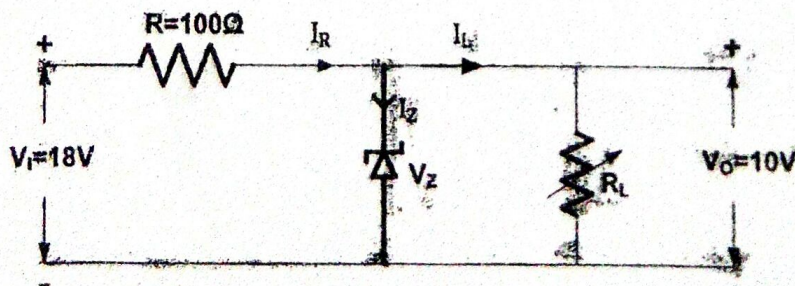- Find the Zener current in the given circuit when  $R_L = 1.2 \text{ K}\Omega$ . Assume  $V_Z = 10 \text{ V}$ . [4]



- Explain the common emitter configuration circuit of npn transistor with the help of input and output characteristics. [6]



8. Explain the working principle of N channel depletion type MOSFET with necessary diagrams. [6]
9. State any four properties of an ideal op-amp. Design a summing amplifier using Op-Amp to get the output voltage  $V_0 = -V_1 + 2V_2 + 3V_3$ . [2+3]
10. Explain how square wave can be generated using Op-Amp and write the relation for frequency of oscillation. [4+1]
11. Define communication system and draw the complete block diagram of communication system. [2+3]
12. What is optical fiber? Explain the advantages of optical fiber communication over traditional communication system. [2+3]
13. Simplify the expression using K-map,  $Y = A'BC' + ABC' + ABC$ . [3]
14. Explain the operation of SR-flip flop with necessary diagrams and characteristics table. [6]
15. (a)  $(10101.101)_2 = (?)_{10}$  (b)  $(9001180)_{10} = (?)_{BCD}$  (c)  $(2AB.5E)_{16} = (?)_8$  [1×3]
16. What is instrumentation system? Explain the instrumentation system with the help of simple block diagram. [1+3]
17. Write short notes of any two: [2×4]
  - a) Data Logger
  - b) DMM
  - c) Strain Gauge

\*\*\*