


Exam.	Back		
Level	BE	Full Marks	80
Programme	BCE, BME, BGE	Pass Marks	32
Year / Part	I / II	Time	3 hrs.

Subject: - Basic Electrical Engineering (EE 451)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) What is electric current? How the concept of electric current was originated. [4]
- b) The filament of a 60W, 230V lamp has a normal working temperature of 2000°C. Take the temperature coefficient to be 0.005 at room temperature 20°C. Find the current which flows at the instant of switching on the supply to the cold lamp. [6]
- c) Define the terms power and energy and state their practical units. What is monthly energy consumption and the monthly electrical charges of using the following electrical equipment at Rs 7 per kWh?
 - (i) Ten 1200Watt heaters for 5 hours
 - (ii) Six 50 Watt TV for 4 hrs.
 - (iii) Five 400 Watt fans for 10 hours.
 - (iv) 4800Watt electric clothes dryer for 2 hours.

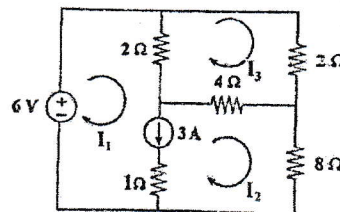
2. a) Using mesh analysis determine the current through all the resistors. [6]



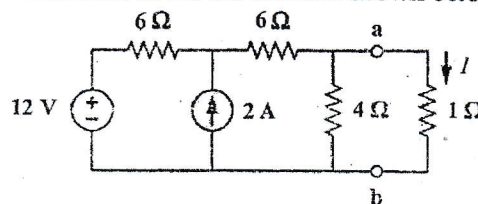- b) Using thevenin's theorem find the current flowing through load resistance of value 1Ω connected across terminals ab for the network shown below. [6]



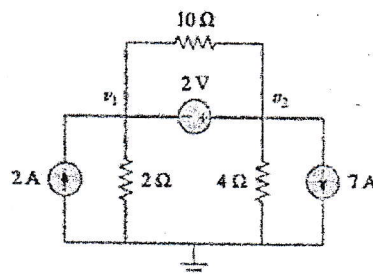- c) Explain reciprocity theorem with example. [4]
3. a) Use nodal analysis to find the current through 4Ω resistor for the network shown below. [8]



- b) Prove the total equivalent inductance of two inductive coils joined in series will be $L_{eq} = L_1 + L_2 - 2M$, where L_1 and L_2 are coefficient of self-inductance of 1st and 2nd coil and M is the coefficient of mutual inductance. [4]
- c) Find the form factor and peak factor of sinusoidal voltage $v = 10 \sin(\omega t)$. [4]
4. a) A coil and non-inductive resistor are connected in series across a 200V, 50Hz supply. The voltages across the coil and resistor are 120V and 140V respectively. If the supply current is 0.5A, calculate (i) the resistance and inductance of the coil; (ii) the power dissipated in the coil; (iii) the power factor of the coil; (iv) the power factor of the circuit. [8]
- b) A RC series circuit ($R_1 = 40\Omega$, $C = 10\mu F$) and RL series circuit ($R_2 = 50\Omega$, $L = 0.2\Omega$) are connected in parallel to each other and a source of 100V, 50Hz is applied across the overall circuit. Calculate (i) current drawn by each branch and overall current taken from supply (ii) power factor of circuit (iii) Active , Reactive and Apparent power [8]
5. a) Three impedances of $(10+j10)\Omega$, $(12+j12)\Omega$ and $(2+j2)\Omega$ are connected in delta to a 3-phase system with line voltage 400V. Calculate all the phase currents, line currents, active powers, reactive powers and apparent power. [8]
- b) How can we measure the power factor angle of the circuit using two wattmeter power measurement method? [8]
