

Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BCE, BME, BGE	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. a) Define ideal current source. Show that if  $\alpha_1$  is the resistance temperature coefficient of a conductor at temperature  $t_1$  °C then resistance temperature coefficient at  $t_2$  °C is given by  $\frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$ . [5]

- b) A coil has a resistance of  $18\ \Omega$  when its mean temperature is  $20^\circ\text{C}$  and of  $20\ \Omega$  when its mean temperature is  $50^\circ\text{C}$ . Find its mean temperature rise when its resistance is  $21\ \Omega$  and the ambient temperature is  $15^\circ\text{C}$ . [5]


- c) Find  $V_{XY}$  in the figure. [5]

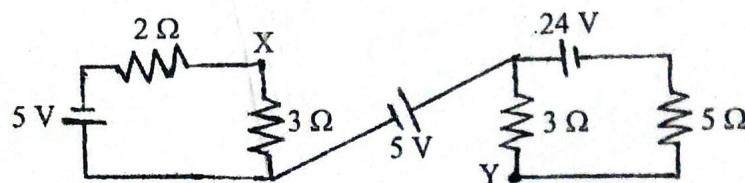

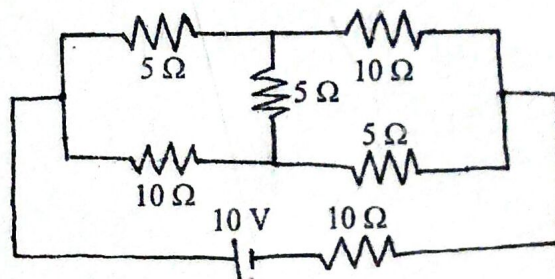
2. a) Find equivalent resistance of the given network. [5]



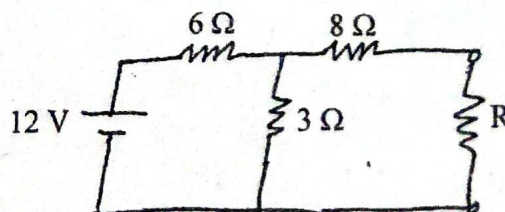- b) Determine the value of  $R$  for maximum power to  $R$  and calculate the power delivered under this condition. [4]



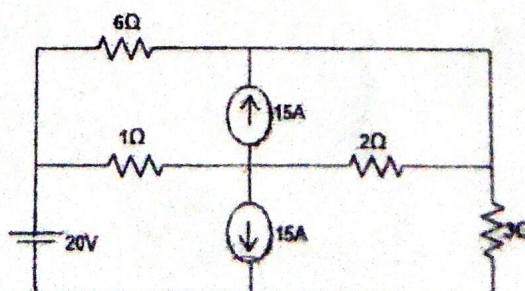- c) Calculate the voltage drop across  $3\ \Omega$  resistor using Superposition Theorem in the circuit given below. [6]






3. a) Explain super node and needs with suitable example. [4]


b) Define capacitance and inductance. Also classify the capacitors on the basis of geometrical shapes. [4]

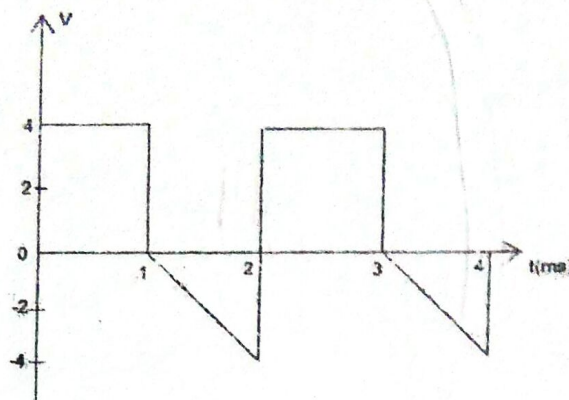c) Calculate the Rms value and Average value of the voltage wave given below and hence compute the form factor. [8]




4. a) Explain the operation of purely capacitive circuit excited by a sinusoidal source and hence prove that average power consumed by such circuit is zero. Draw necessary waveforms. [6]

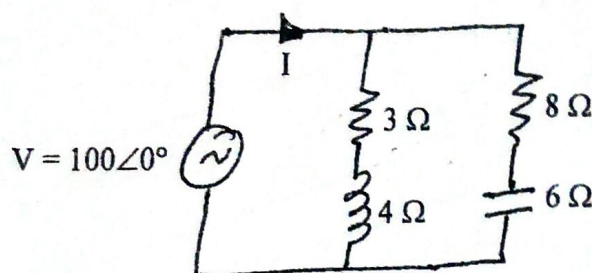b) For the circuit given below, calculate the current I. Draw the phasor diagram of the circuit. [6]



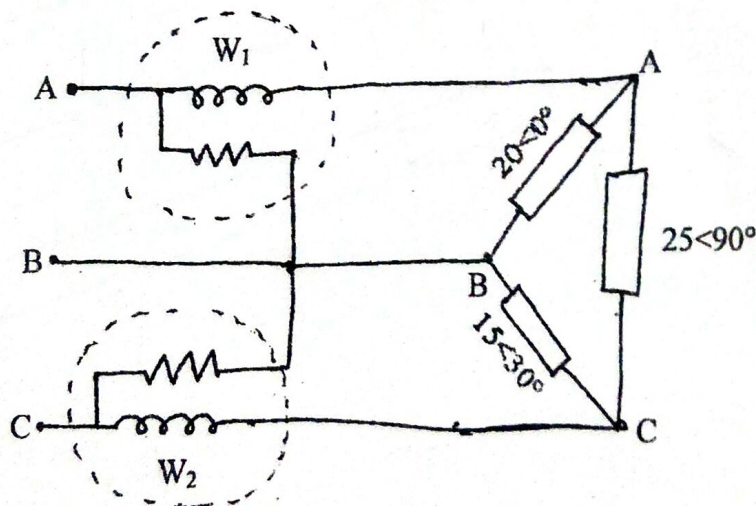c) The supply system is 230 V, 3-phase, 50 Hz. Determine the readings of wattmeters  $W_1$  and  $W_2$ . Phase sequence is AB-BC-CA. [7]



5. a) Derive the equation for the instantaneous current when A.C. voltage is supplied to a series R-L circuit. Draw phasor diagrams and analyze power in the circuit. [6]

b) Calculate the amount of current through the neutral of a balanced 3-phase star connected circuit. Also verify with the phasor diagram. [3]

c) An electric circuit is being supplied by an a.c. source of 100 V rms. The circuit has a resistance of  $10\ \Omega$ , inductor of  $12\ \Omega$  reactance and capacitance of  $8\ \Omega$  reactance connected in series. Compute the active power and power factor of the circuit. [6]