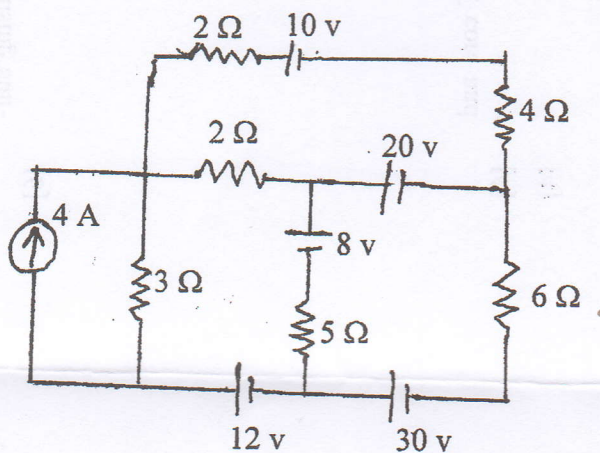


Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) Differentiate between Practical Voltage Source and Practical Current Source. [4]
- b) The field winding of dc motor takes 1.15 A current at 20°C. If current falls to 0.26 A after working for some hours, supply voltage remaining constant, find the final working temperature of field winding. Given,  $\alpha_0 = \frac{1}{234.5}$  and voltage = 230V. [6]
- c) Three lamps of rating 220 V and 150 watt, 200 watt and 450 watt are connected across 200 V supply. Calculate the resistance of each lamp and the power consumed by each lamp at 200 V. [6]
2. a) Solve the given network with mesh analysis to find voltage drop on 5  $\Omega$  resistors. [6]



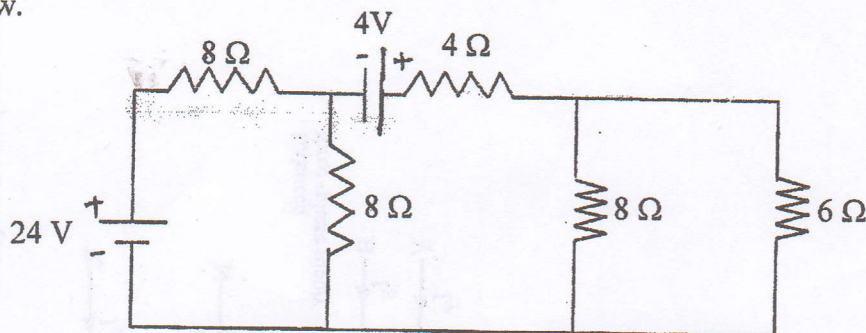- b) Use nodal analysis to find the current through 4 $\Omega$  resistor for the network shown below. [6]




- c) State and explain superposition theorem with suitable example. [4]




3. a) Using thevenin's theorem find the current through the  $4\Omega$  for the network shown below.

[6]

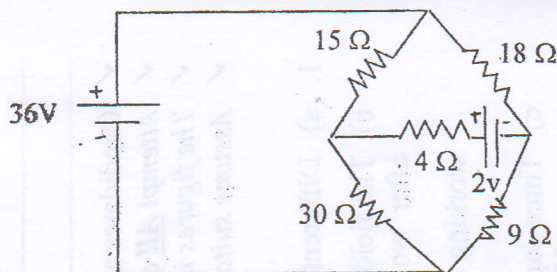

- b) Determine the power dissipated in the  $8\Omega$  resistor of the given network using star-delta and delta-star transformation.

[6]

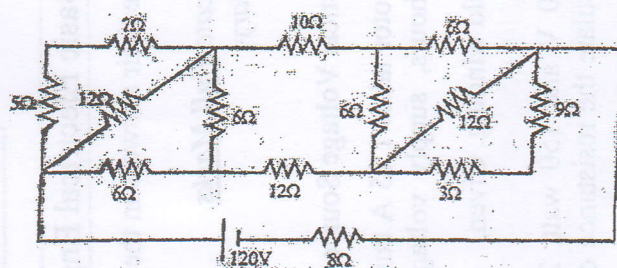


- c) How mutual inductance between two coils depends upon dimensions of core and coils.

[4]

4. a) Find the form factor and peak factor of the current waveform given below.

[4]

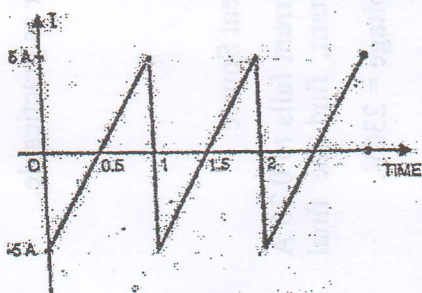


- b) A coil of inductance  $318.3 \text{ mH}$  is connected in series with a  $200\Omega$  resistor to a  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate the current flowing, power factor, active and reactive power of the circuit. Also draw the phasor diagram.

[6]

- c)  $Z_1 = (40 - j318.31)$  and  $Z_2 = (50 + j62.83)$  are connected in parallel to each other and a source of  $100 \text{ V}$ ,  $50 \text{ Hz}$  is applied across the overall circuit. Calculate (i) circuit current (ii) Active, reactive and apparent power.

[6]

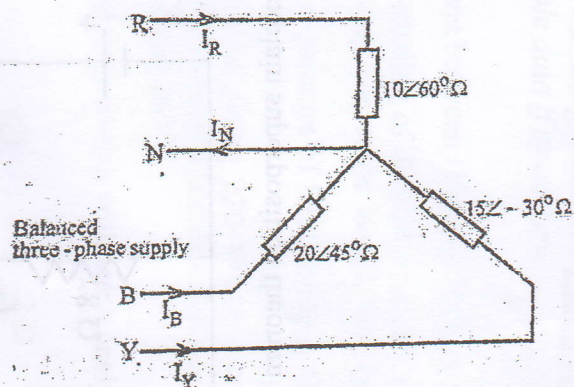5. a) Discuss the effect of low power factor. A single phase load of 7Kw operates at a power factor 0.7 lagging. It is proposed to improve the power factor to 0.9 lagging by connecting a capacitor the load. Calculate the KVAR rating of the capacitor. [3+5]
- b) For the following unbalanced system with balanced three phase supply of 400 V, 50 Hz, calculate: [8]
- The line currents and neutral current
  - Active and reactive power absorbed by the circuit
  - Draw the phasor diagram.



\*\*\*