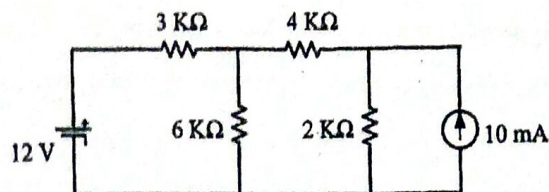


| Exam. | New Back (2066 & Later Batch) | | |
|-------------|-------------------------------|------------|--------|
| Level | BE | Full Marks | 80 |
| Programme | All (Except B.Arch) | Pass Marks | 32 |
| Year / Part | I / II | Time | 3 hrs. |

Subject: - Basic Electronics Engineering (EX451).

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.


1. State Thevenin's theorem and use it to find the current through 4 kΩ resistor. [1+5]



2. Explain the operation of RC low pass filter with its transfer function and frequency response. [4]

3. What is diode? Explain the I-V characteristics of PN junction diode. [1+4]

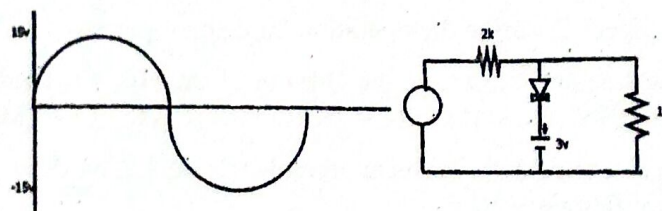4. Define pulse shaping circuits. Find the output wave form of the given circuit. [1+4]



5. Draw emitter feedback bias circuit of BJT by labeling all the circuit components. Find I_C and V_{CE} in the circuit if $V_{CC} = +12V$, $R_B = 430 k\Omega$, $R_C = 2 k\Omega$, $R_E = 1 k\Omega$ and $\beta = 50$. [2+3]

6. Draw the structure of CMOS. Describe the operation of CMOS logic inverter. [5]

7. Explain the concept of virtual ground. Design a summer circuit using op-amp to get the output voltage as: $V_0 = -(V_1 + 10V_2 + 25V_3)$ [1+4]

8. Define positive feedback. Draw the circuit diagram for Wien Bridge oscillator and explain the principal of operation. [1+4]

9. Draw a block diagram of communication system and explain each block briefly. [6]

10. Write short note on optical fiber. What are the advantages of optical fiber communication over traditional communication system? [2+2]

11. State and prove De-Morgan's theorems. [4]

12. Explain the operation of SR flip-flop with necessary diagram. [5]

13. Convert the following number system. [3]

(a) $(25.5)_{10} = (?)_2$ (b) $(EAB)_{16} = (?)_{10}$ (c) $(9180)_{10} = (?)_{BCD}$

14. Write short notes on: (any two) [2×5]

- a) Strain Gauge
- b) Data Logger
- c) DMM

15. Describe the construction and working principal of N-channel Depletion type MOSFET. [8]