


2068 Chaitra

Exam.	Level	Programme	Year / Part	Full Marks	Pass Marks	Time
	BE	BEL, BEX, BCT, BIE, B. Agri.	1 / 1	80	32	3 hrs.


Subject: - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any **Five** questions.
- ✓ The figures in the margin indicate **Full Marks**.
- ✓ Assume suitable data if necessary.

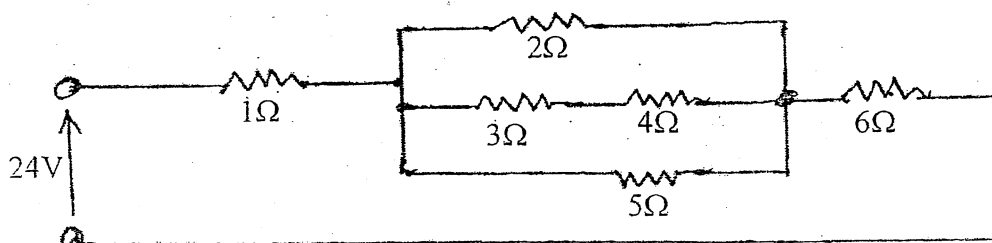1. a) Explain emf, potential difference and current with a circuit diagram. [4]
- b) The temperature rise of the machine field winding was determined by the measurement of the winding resistance at 20°C the field winding resistance was 160 Ohm(Ω). After running the machine for some hours at full load the resistance is 185 Ω . If the temperature coefficient of resistance of the copper winding is $4.3 \times 10^{-6}/^{\circ}\text{C}$ at 0°C. Determine the temperature rise of the machine. [6]
- c) Find the equivalent resistance in the figure shown, and power dissipated in the 5 Ω resistor. [6]



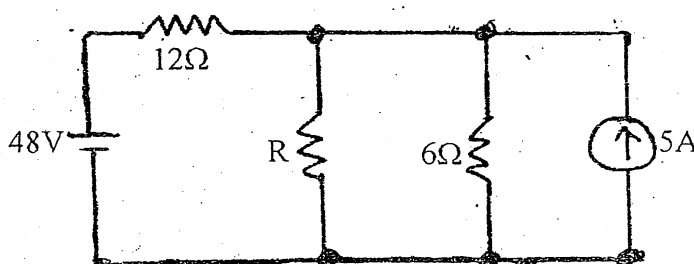
2. a) Calculate the value of R that will absorb maximum power from the circuit (shown in the figure). Also calculate the maximum power drawn by it. [6]




- b) State Norton's description theorem and list the steps for Nortonizing a circuit. Compare the Norton's equivalent circuit to the Thevenin's equivalent circuit. [6]
- c) What is the total cost of using the following at Rs 7 per kallowatt hour? [4]
 - i) A 1200 W toaster for 30 min
 - ii) Six 50 W bulbs for 4 hours

- iii) A 400 W washing machine for 45 min.
iv) A 4800 W electric cloths dryer for 20 min.

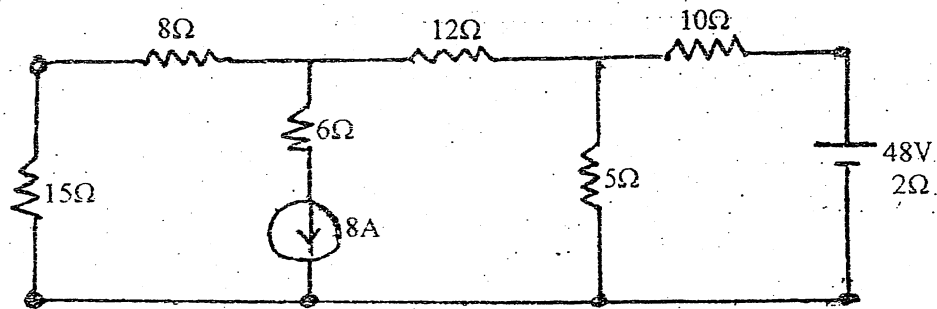
3. a) Use Nodal analysis method to calculate the current through the 15Ω resistor in the figure shown below. [8]



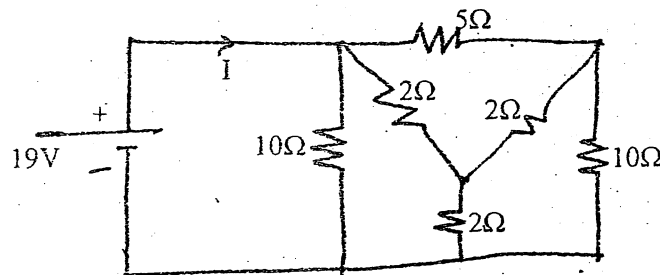- b) Find the current I as shown in figure below using star - delta transformation. [4]



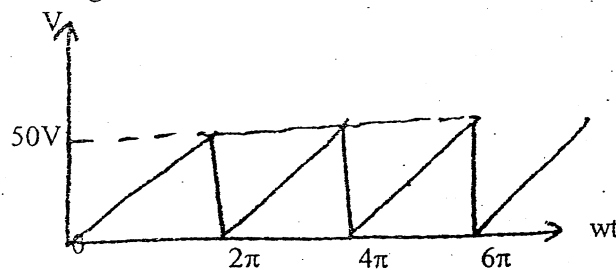- c) An air cored coil is 2.5cm long and has an average cross-sectional area of 2cm^2 . Determine the number of turns if the coil has an inductance of $100\mu\text{H}$. [4]
4. a) Calculate the average value, rms value, form factor and peak factor of the saw tooth wave as shown in figure below. [6]



- b) What do you mean by reactive power in AC circuit? Explain it by constructing phasor diagram for real power, reactive power and apparent power. [5]
c) Describe and illustrate the phasor relationship that exist between the voltage that appears across the terminals of a pure capacitor and the current that flows through it in steady state when the capacitor is excited by a sinusoidal source. [5]
5. a) A voltage of $200\angle 0^\circ\text{ V}$ is applied across impedances in parallel. The value of impedances are $(12 + j16)\Omega$ and $(10 - j20)\Omega$. Determine the KW, KVA and KVAR in each branch and the power factor of the whole circuit. [8]
b) A delta connected load of $Z_{AB} = 52\angle 45^\circ\Omega$, $Z_{BC} = 52\angle -30^\circ\Omega$ and $Z_{CA} = 10\angle 0^\circ\Omega$ are connected to a 380V, 3 phase ac source. Find the magnitude of the line currents and total power absorbed by loads, when phase sequence is ABC. [8]

- [8] a) A single phase motor takes a current of 40A at pf 0.7 lagging from a 440V, 50HZ supply. What value must a shunting capacitor have to raise the power factor to 0.9 lagging. [6]
- b) What are the advantages of three phase AC system over single phase ac system? [4]
- c) Determine current in 5Ω resistor by mesh analysis in figure below. [6]

