


TRIBHUVAN UNIVERSITY
INSTITUTE OF ENGINEERING
Examination Control Division
2076 Bhadra

Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	ALL Except BEI, BAR	Pass Marks	32
Year / Part	I / II	Time	3 hrs.


Subject: - Basic Electronics Engineering (EX 451)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt **All** questions.
- ✓ The figures in the margin indicate **Full Marks**.
- ✓ Assume suitable data if necessary.

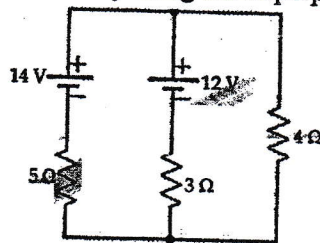1. What is filter? Explain High Pass Filter. [1+3]
2. Find the voltage across the 4Ω resistor by using the Superposition theorem. [6]



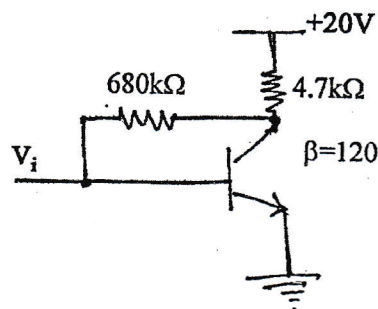3. Explain the operation of photo diode. Draw the circuit diagram of fullwave bridge rectifier. [4+2]
4. Show the relationship between current gain alpha (α) and beta (β) of BJT. Explain the importance of dc loadline analysis in transistor biasing to find collector current & collector emitter voltage. [2+3]
5. Differentiate between depletion and enhancement type MOSFET. Explain NMOS as a switch. [2+4]
6. Determine I_{CQ} and V_{CEQ} for the following circuit. [5]



7. Explain how square wave is generated at output terminal using Op-Amp circuit as square wave generator and draw the circuit diagram of triangular wave generator. [4+2]
8. Show the concept of positive feedback with suitable block diagram. Draw the circuit diagram of Wein Bridge Oscillator using Op-amp. [3+2]
9. Design a summer circuit using op amp as: $V_o = -5V_1 - 10V_2 - 15V_3$
Where, V_o is an output voltage and V_1 , V_2 & V_3 are input voltages. [5]
10. Differentiate between internet and intranet. How Light-propagates through Optical fiber? [2+3]

11. Why modulation is needed? Differentiate AM and FM. [2+3]
12. Differentiate between SR and JK flip-flop. Explain Master-Slave flip-flop with block diagram. [1+3]
13. Simplify using Boolean Algebra. [3×2]
- a) $AC + ABC + \bar{A}(C + A\bar{C})$
 - b) $(A + B)(\bar{A} + B)(A + \bar{B})$
 - c) Subtract $(20)_{10}$ from $(3)_{10}$ using 1's complement method
14. Simplify the function using K-map:
 $F(D, C, B, A) = \Sigma(3, 4, 5, 7, 9, 13, 14, 15)$ and realize this circuit using gates. [6]
15. Write short notes on: (*Any Two*) [3×2]
- a) Data logger
 - b) Regulated power supply
 - c) Transducer
